

HW1 (208 points in total)

1. Convert the following binary numbers to decimal: (20 points)

- (1) 1011
- (2) 1000
- (3) 1111
- (4) 10101.11

2. Convert the following decimal numbers to binary: (20 points)

- (1) 10
- (2) 8
- (3) 16
- (4) 52
- (5) 12.625

3. (a) Convert to hexadecimal: 100101.101_2 . (10 points)

(b) Convert to binary: $DEC.A_{16}$.

4. Prove the following theorems algebraically: (20 points)

(a) $X(X'+Y)=XY$

(b) $X + XY = X$

(c) $XY + XY' = X$

(d) $(A + B)(A + B') = A$

5. Prove the law/theorem is being used: (15 points)

(a) $(X+Y)(X+Z)=X+YZ$

(b) $(X+Y)(X'+Z)=XZ+X'Y$

(c) $XY+X'Z+YZ=XY+X'Z$

6. Complete the following logic expressions: (8 points)

$AxA=$ $Ax0=$ $Ax1=$ $AxA' =$

$A+A=$ $A+0=$ $A+1=$ $A+A' =$

7. Complete the following logic expressions: (10 points)

$A \times A \times A \times A =$

$A \times 1 \times 0 \times B =$

$((A + A) \times A) + A =$

$A + 1 + A + B + 0 =$

$(A \times A) + (A + A) =$

$1 + 1 =$

$A' + A + A' =$


$(A' + A) \times A =$

HW1 (208 points in total)

$$A' \times (A + A \times B) \ 0 \times 0 =$$

$$1 + 0 =$$

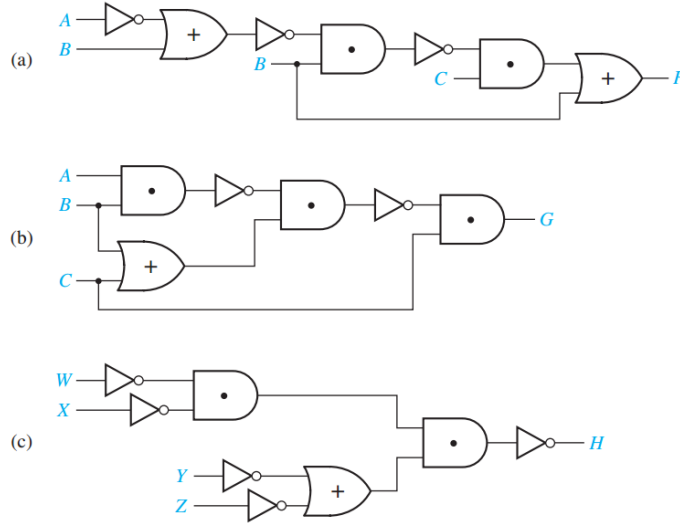
8. Find logic expressions of F, G, H and simplify: (15 points)



9. Summarize the truth table for the following logic gates: (draw the truth table, inputs: A, B, output: F, also draw their gate symbols). (30 points)

AND, OR, NAND, NOR, XOR, XNOR

**Example: AND

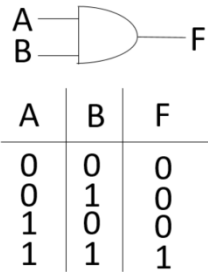

10. Provide the SOP and POS, and the equivalent logic gate circuitry of those expressions for the truth table: (20 points)

HW1 (208 points in total)

| X | Y | Z | F |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

11. Add the following numbers in binary using 2's complement to represent negative numbers. Indicate if an overflow occurs. (20 points)

- (a) In a 6-bit computer system, $21+11$
- (b) In a 6-bit computer system, $(-14)+(-32)$
- (c) In a 6-bit computer system, $(-25)+18$
- (d) In a 5-bit computer system, $(-12)+13$

12. Design a regular 2-4 decoder from the following truth table. Draw the gate level digital circuit from the design. (10 points)

| A | B | Y1 | Y2 | Y3 | Y4 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

13. Design a decoder circuit from the following truth table. (10 points)

| A | B | Y1 | Y2 | Y3 | Y4 |
|---|---|----|----|----|----|
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |