


Equivalent Circuit Theorems - Part 1

① Thevenin's Theorem

Any linear circuit can be simplified to:




EX 1:

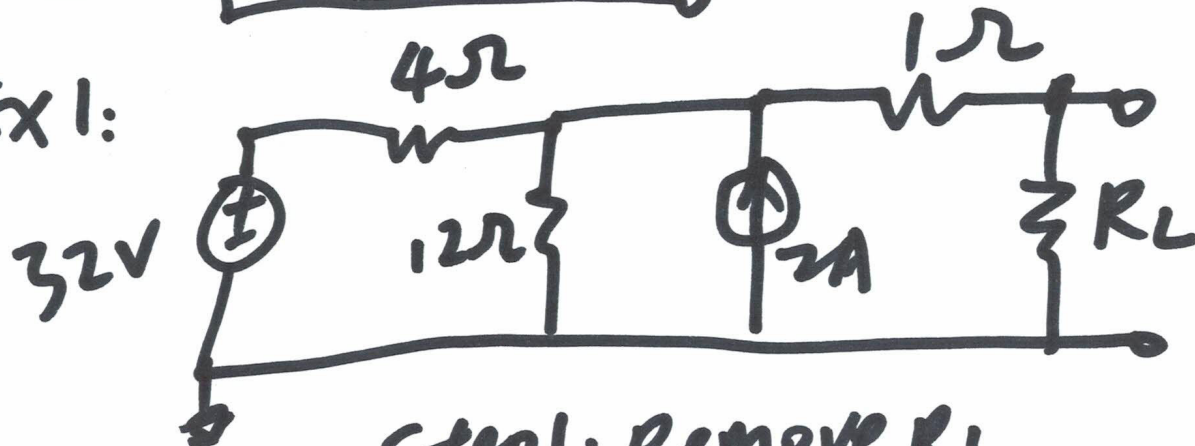

For R_{TH} :

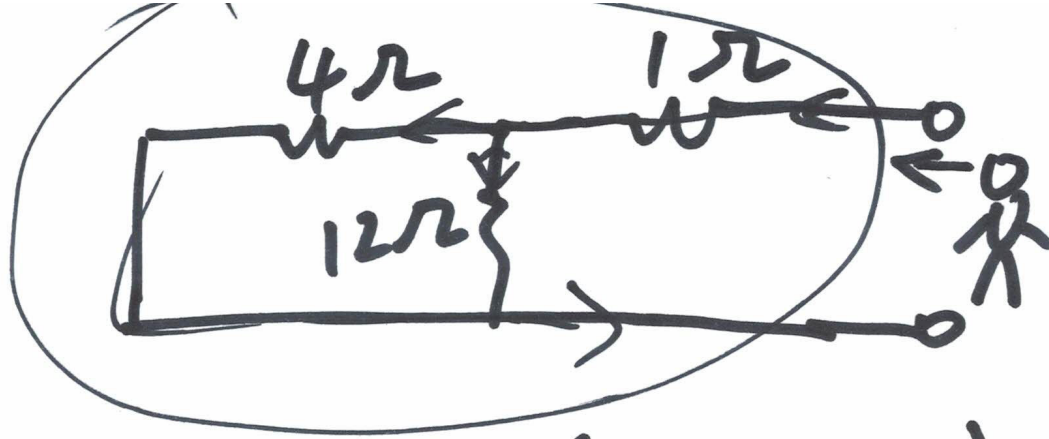
- Step 1: Remove R_L
- Step 2: Short voltage source / disconnect the current source
- Step 3: Get R_{TH}



$$R_{TH} = 1\Omega + (4\Omega \parallel 12\Omega)$$

$$= 1 + \frac{4 \cdot 12}{4 + 12} = 4\Omega$$

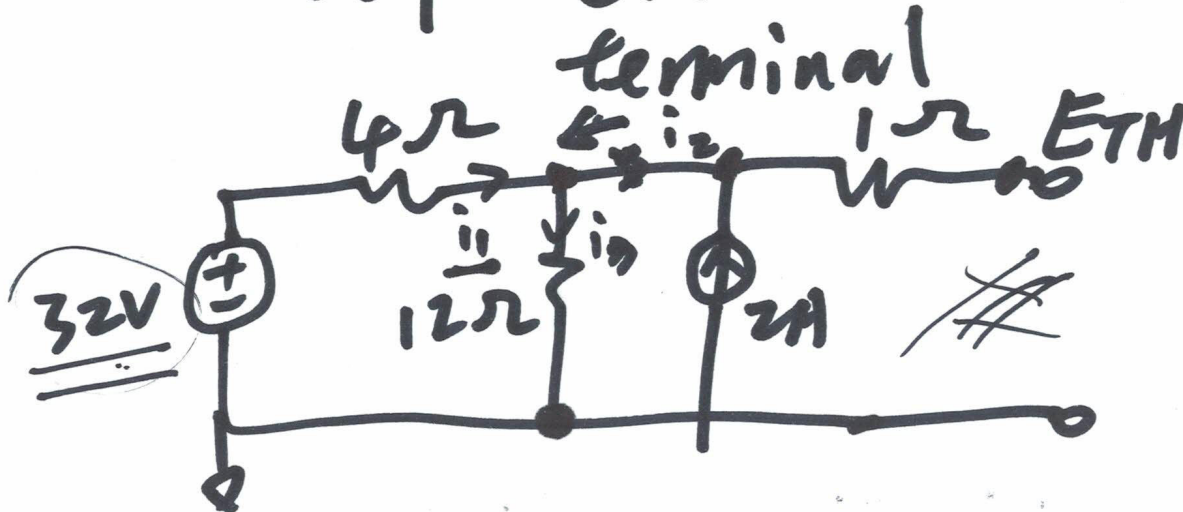For E_{TH} :
 Step 1: REMOVE R_L
 Step 2: E_{TH} is the voltage at the output terminal



$$\begin{cases} i_1 + i_2 = i_3 & \textcircled{1} \\ i_2 = 2 & \textcircled{2} \\ \frac{32 - E_{TH}}{4} + 2 = \frac{E_{TH}}{12} & \textcircled{3} \end{cases}$$

From $\textcircled{3}$ $96 - 3E_{TH} + 24 = E_{TH}$

$$E_{TH} = \frac{120}{4} = 30 \text{ V}$$

∴ the Thevenin's equivalent circuit is:

