

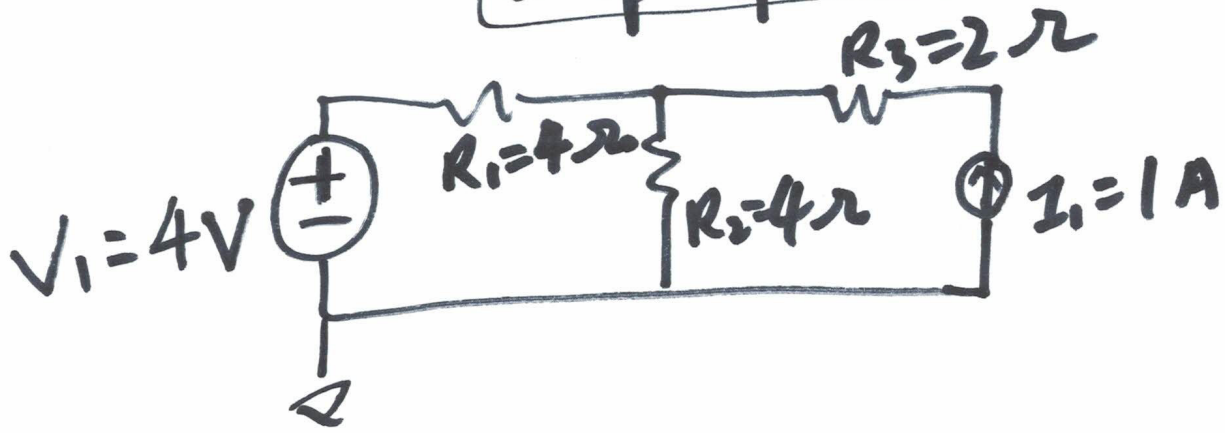


Superposition - Part 3

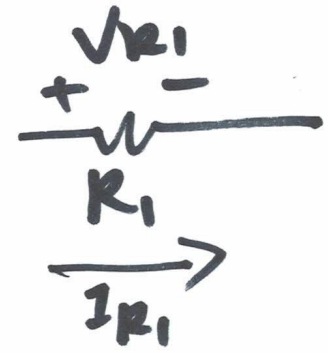

① V_1 only

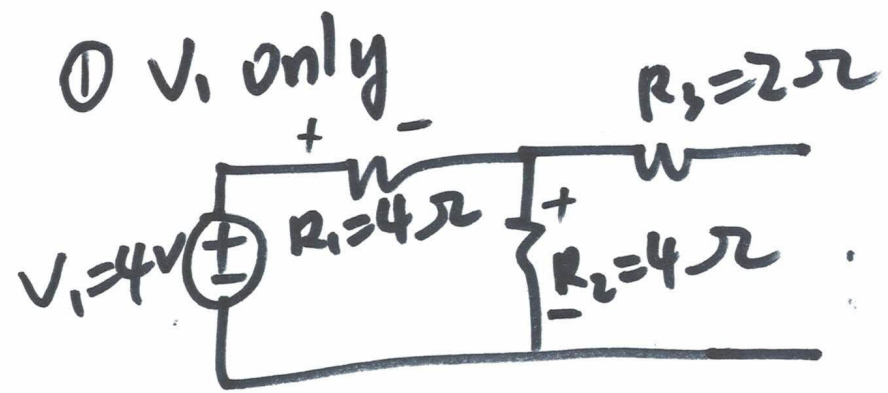


$$V_{R1} = V_1 \cdot \frac{4}{4+4}$$

$$= 2V$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{2V}{4\Omega}$$

$$= 0.5A$$

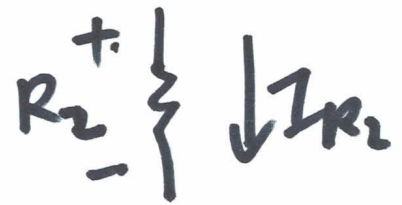



$$V_{R2} = V_1 \cdot \frac{4}{4+4}$$

$$= 2V$$

$$I_{R2} = \frac{V_{R2}}{R_2}$$


$$= \frac{2V}{4\Omega} = 0.5A$$

② I_1 only

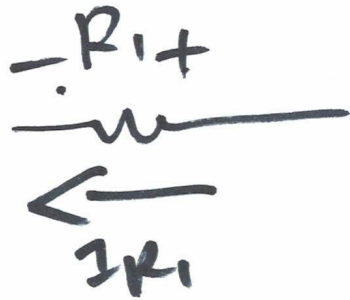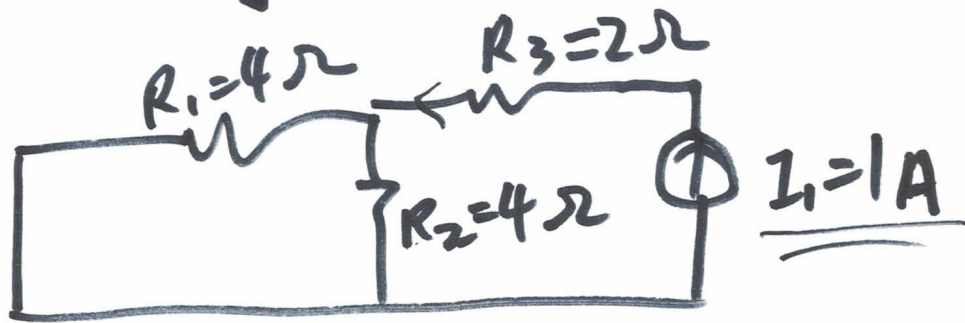


$$V_{R_1} = 0.5A \cdot 4\Omega = 2V$$

$$I_{R_1} = 0.5A$$

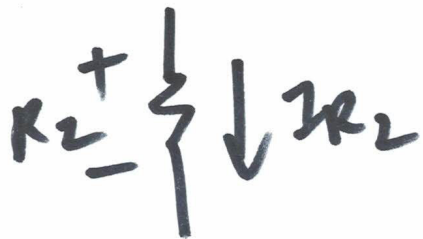

$$V_{R_2} = 0.5A \cdot 4\Omega = 2V$$

$$I_{R_2} = 0.5A$$

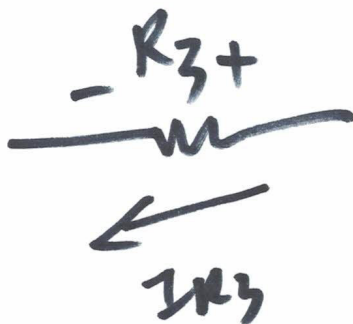

$$V_{R_3} = 1A \cdot R_3 = 1 \cdot 2 = 2V$$

$$I_{R_3} = 1A$$

②

so in total:

$$V_{R_1} = 2V - 2V = 0$$
$$I_{R_1} = \frac{V_{R_1}}{R_1} = 0A$$

$\xrightarrow{+R_1}$
—
 \rightarrow
 I_{R_1}

$$V_{R_2} = 2V + 2V = 4V$$
$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{4V}{4\Omega} = 1A$$

$I_{R_2} \downarrow$ $\left\{ \begin{array}{l} + \\ - \end{array} \right.$ R_2

$$V_{R_3} = 2V$$
$$I_{R_3} = 1A$$

$-R_3+$
—
 \leftarrow
 I_{R_3}

(3)