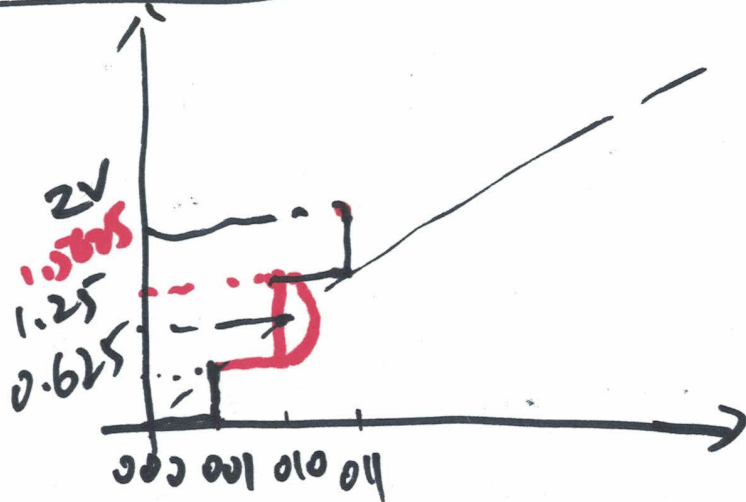


HW 2 Review

Digital Input	Vout	Ideal Vout
000	0V \downarrow	0V \downarrow
001	0.625V	0.625V
010	1.5625V	1.25V
011	2V	1.875V
100	2.5V \uparrow	2.5V
101	3.125V	3.125V
→ 110	3.4375V	3.75V
111	4.375V	4.375V



$$DNL_2 = \frac{1.5625 - 0.625}{0.625} - 1 \text{LSB}$$

$$= 0.5 \text{LSB}$$

$$DNL_3 = \frac{2V - 1.5625}{0.625} - 1 \text{LSB}$$

$$= -0.3 \text{LSB}$$

$$DNL_4 = \frac{2.5 - 2}{0.625} - 1 \text{LSB}$$

$$= -0.2 \text{LSB}$$

$$DNL_6 = \frac{3.4375 - 3.125}{0.625} - 1 \text{LSB}$$

$$= -0.5 \text{LSB}$$

$$DNL_7 = \frac{4.375 - 3.4375}{0.625} - 1 \text{LSB}$$

$$= 0.5 \text{LSB}$$

$$INL_2 = \frac{1.5625 - 1.25}{0.625} = 0.5 \text{ LSB}$$


$$INL_3 = \frac{2 - 1.875}{0.625} = 0.2 \text{ LSB}$$

$$INL_6 = \frac{3.4375 - 3.75}{0.625} = -0.5 \text{ LSB}$$

~~INL~~

(2)



MOSFETS

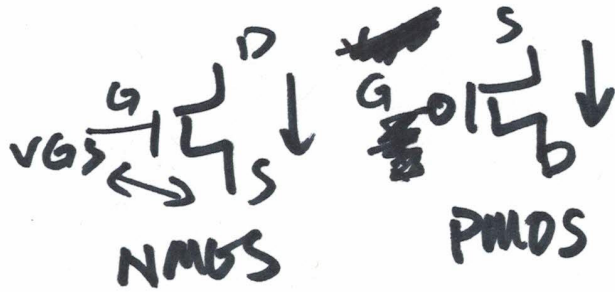

CMOS
 \Rightarrow complementary

$V_{GS} > V_{THN}$
 $V_{GS} - V_{THN} > 0$
 NMOS is good
 at passing 0's
 but not 1's.

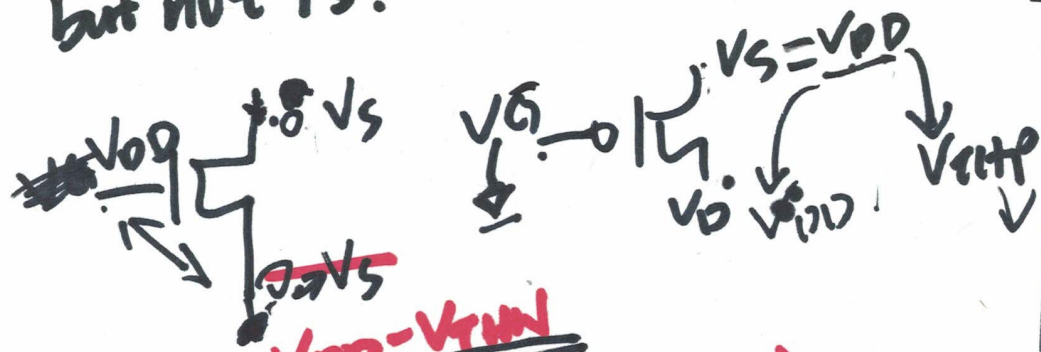
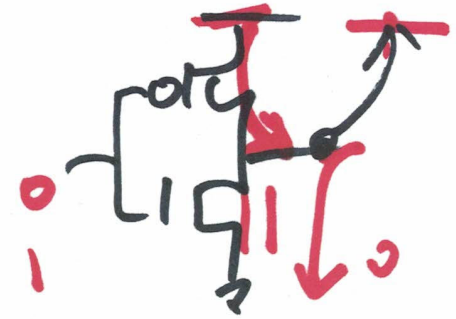
$V_{GS} > V_{THP}$
 PMOS is good
 at passing 1's
 but not 0's



$V_{GS} = V_{DD} - (V_{DD} - V_{THN})$
 $= V_{DD} - V_{THN}$

NAND




A	B	$Y = \overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

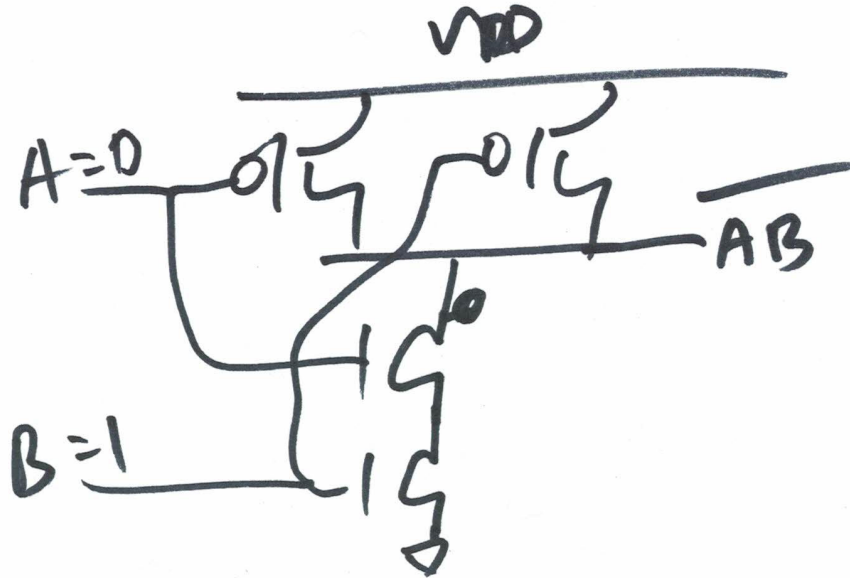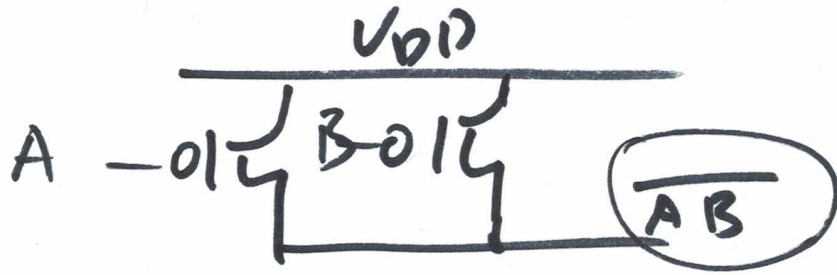

4



11

$Y = A \cdot B \cdot C$

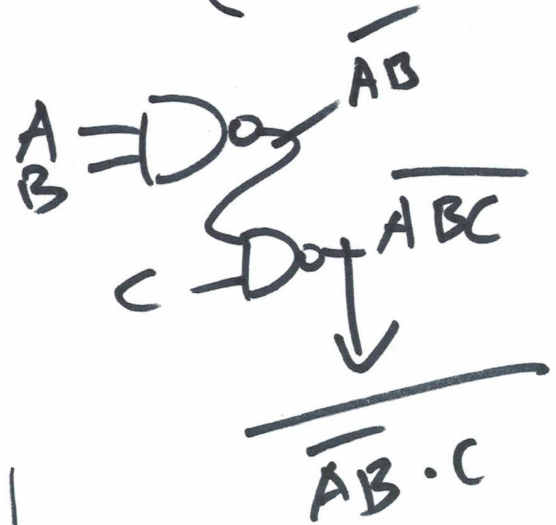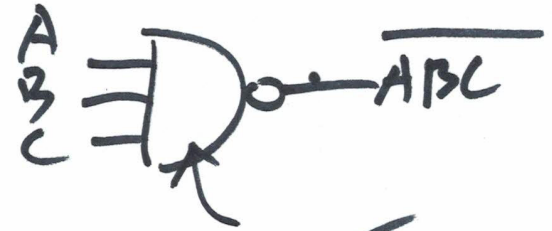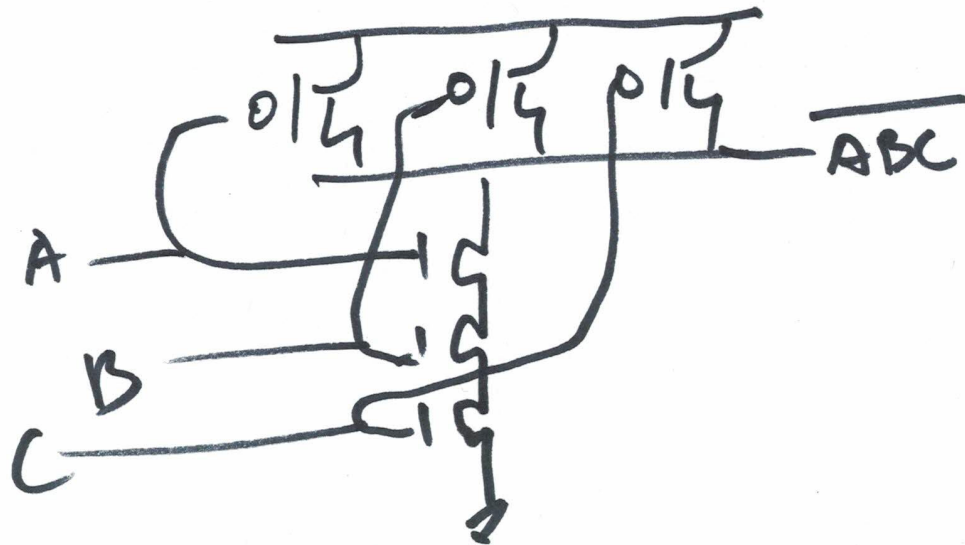

AOI Logic

AND
OR
Invert

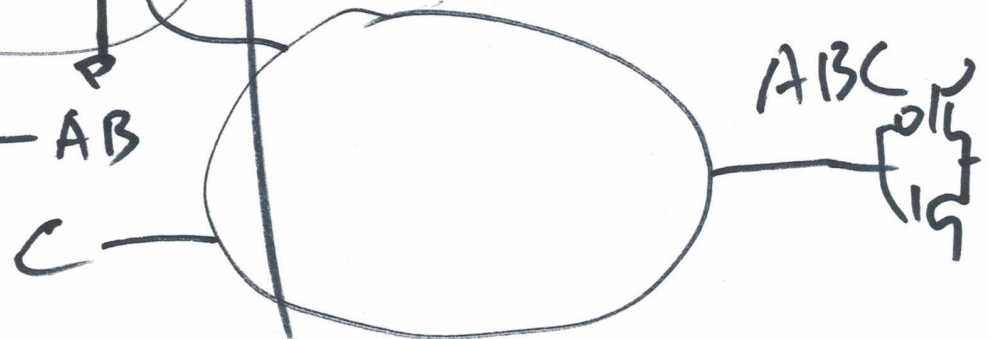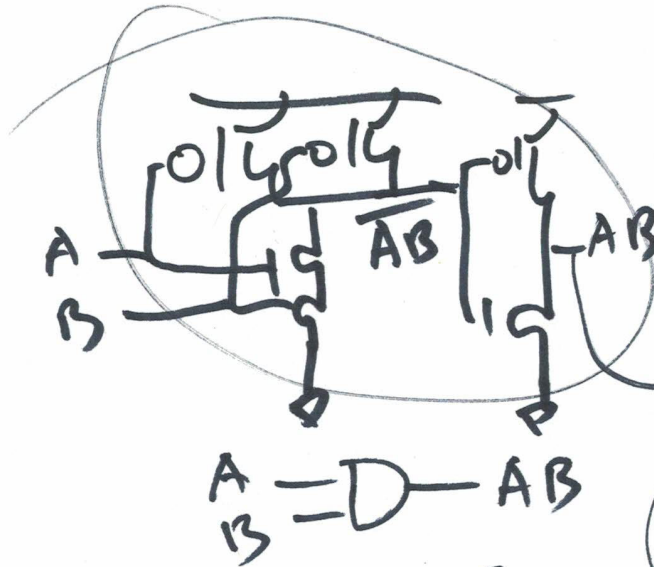


5

$$Y = \bar{A} + BC$$

$$= \overline{\bar{A} + BC}$$

$$= \bar{\bar{A}} \cdot \overline{BC}$$

$$= A \cdot (\bar{B} + \bar{C})$$

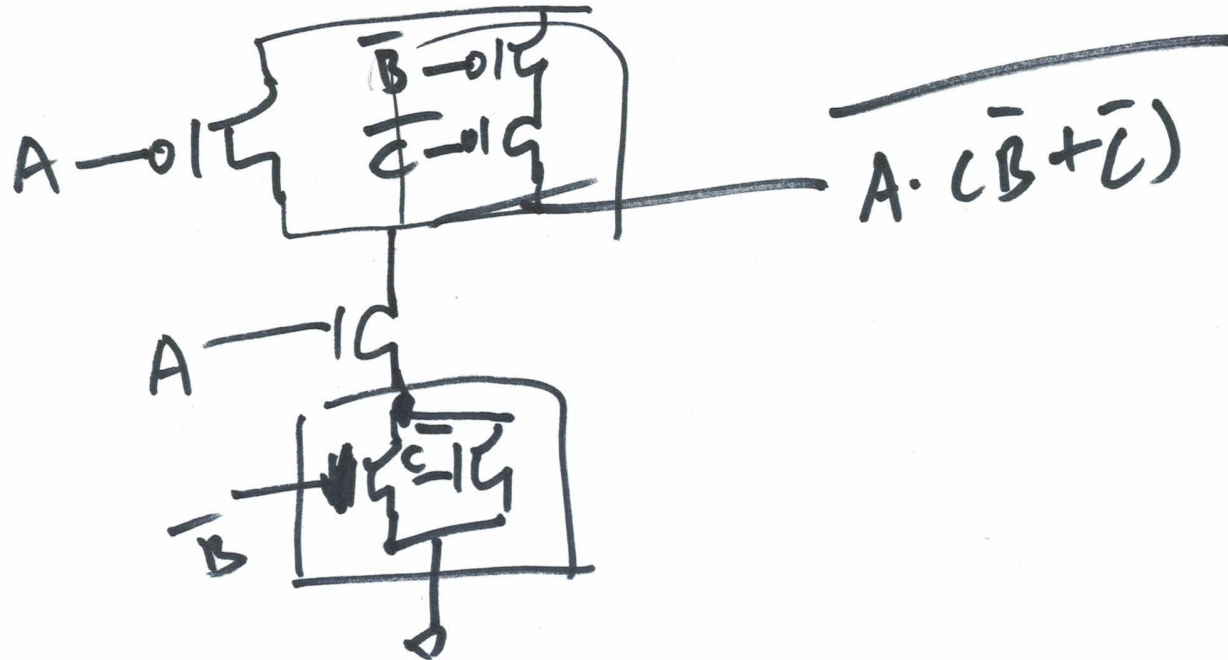

(b)