
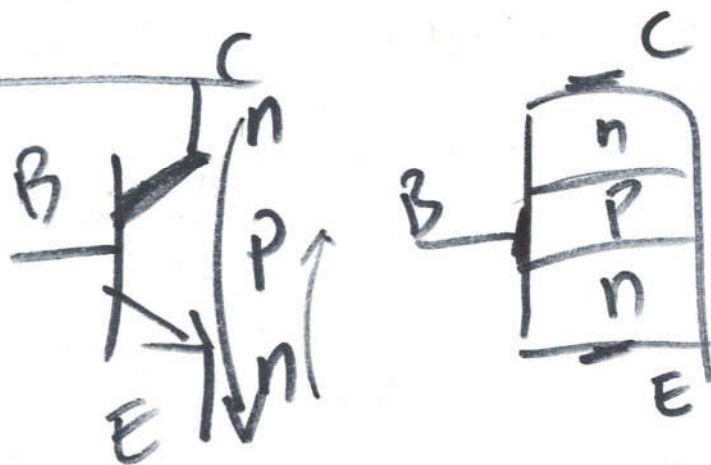


More of BJTs

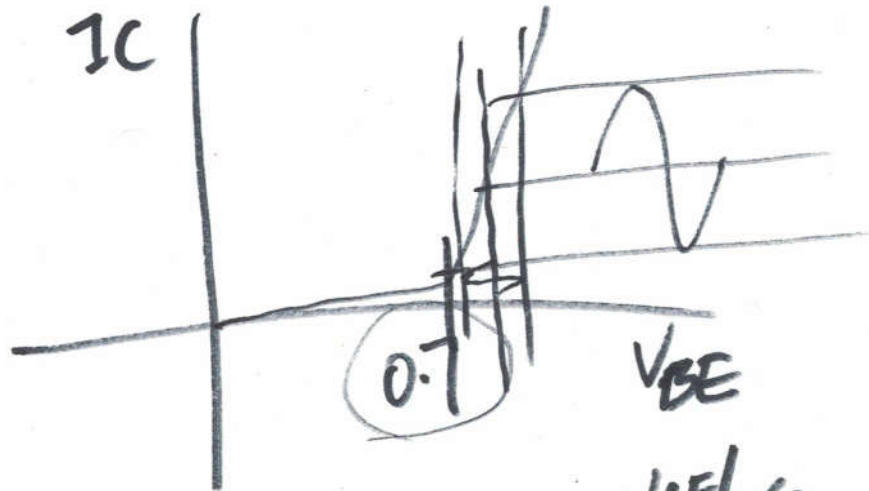

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow \frac{I_C}{I_S} = e^{\frac{V_{BE}}{V_T}} \Rightarrow \ln \frac{I_C}{I_S} = \ln e^{\frac{V_{BE}}{V_T}}$$

$$\Rightarrow \ln \frac{I_C}{I_S} = \frac{V_{BE}}{V_T}$$


$$\Rightarrow \frac{V_{BE}}{V_T} = \ln \frac{I_C}{I_S}$$

V_T : thermal voltage

25 mV at room temperature

I_S : Saturation current

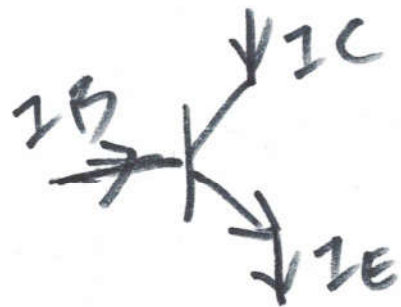- junction area
- base width
- temperature.



$$I_E = I_C + I_B$$

$$I_C = \beta I_B$$



$$I_E = \alpha I_C \approx I_C$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\beta = 50, 100, 200$$

$$\alpha = 0.9 \dots$$

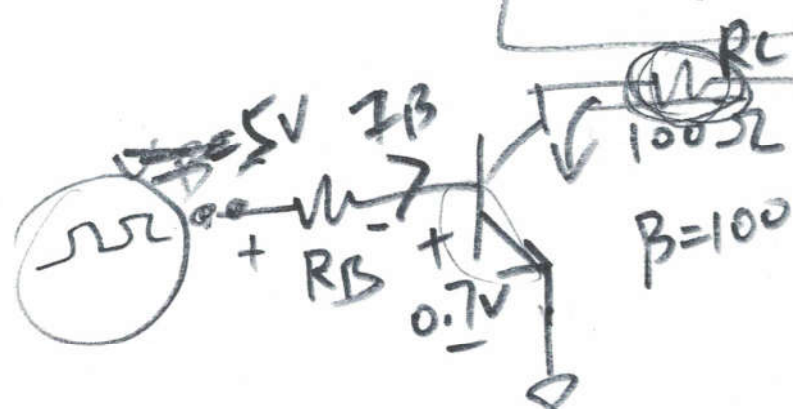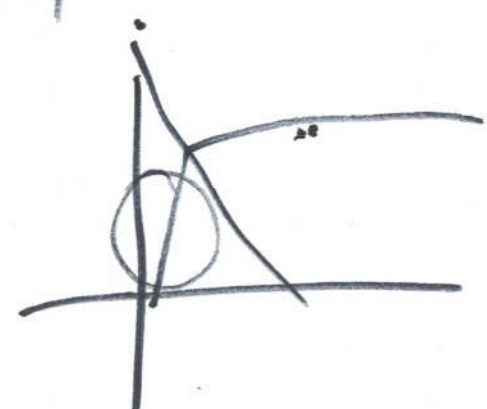

① If R_B is too small, blows up the BJT.

② If R_B is too large, BJT is off

If $R_B = 1k\Omega$, $V_{RB} = 5 - 0.7 = 4.3V$

$$I_B = \frac{V_{RB}}{R_B} = \frac{4.3V}{1k\Omega} = 4.3mA$$



$$I_C = \beta \cdot I_B = 100 \cdot 4.3mA = \underline{430mA}$$

$$V_{RC} = \frac{15V}{1\Omega} \cdot 430mA$$

$$= 43000mV$$

$$= \underline{43V}$$

②

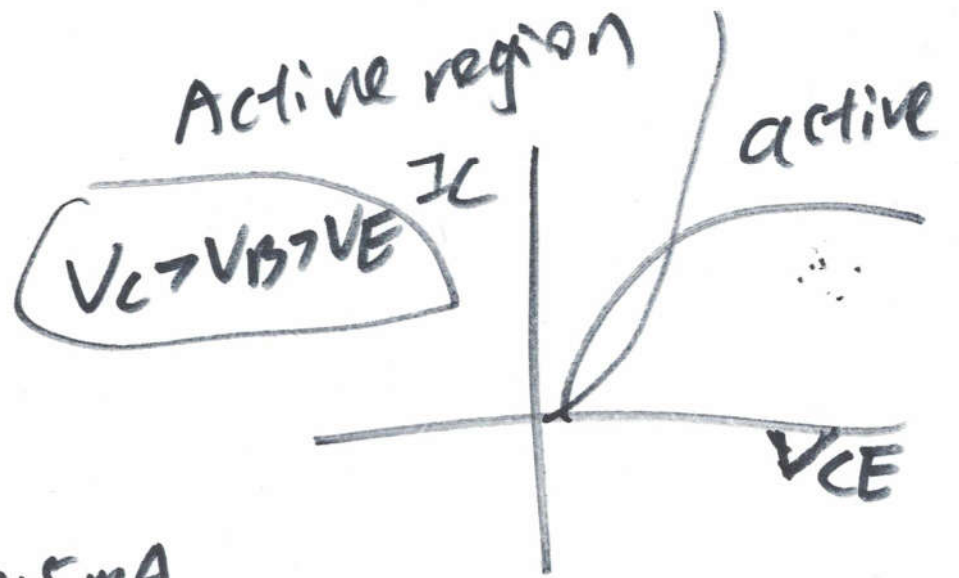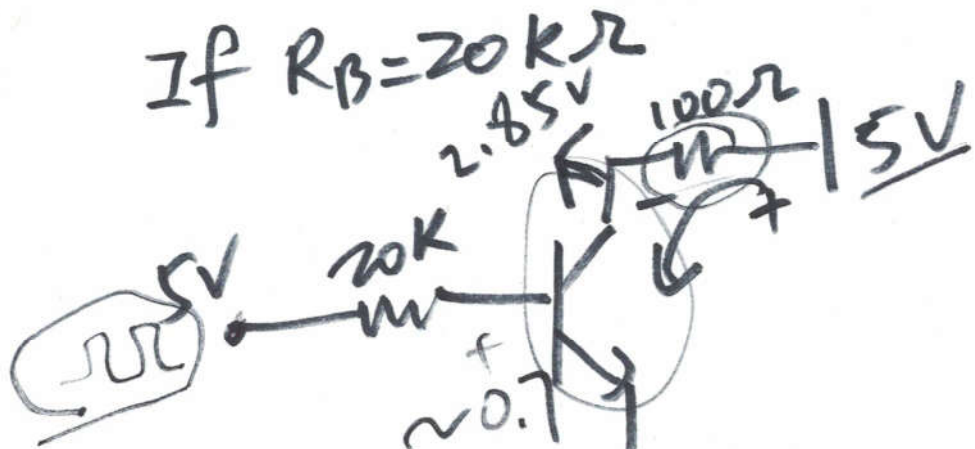



$$I_B = \frac{5V - 0.7V}{20k} = \frac{4.3V}{20k} = 0.215mA$$

$$I_C = \beta \cdot I_B = 100 \cdot 0.215mA = 21.5mA$$

$$V_{RC} = I_C \cdot R_C = 100\Omega \cdot 21.5mA = 2150mV = \underline{2.15V}$$

741


3

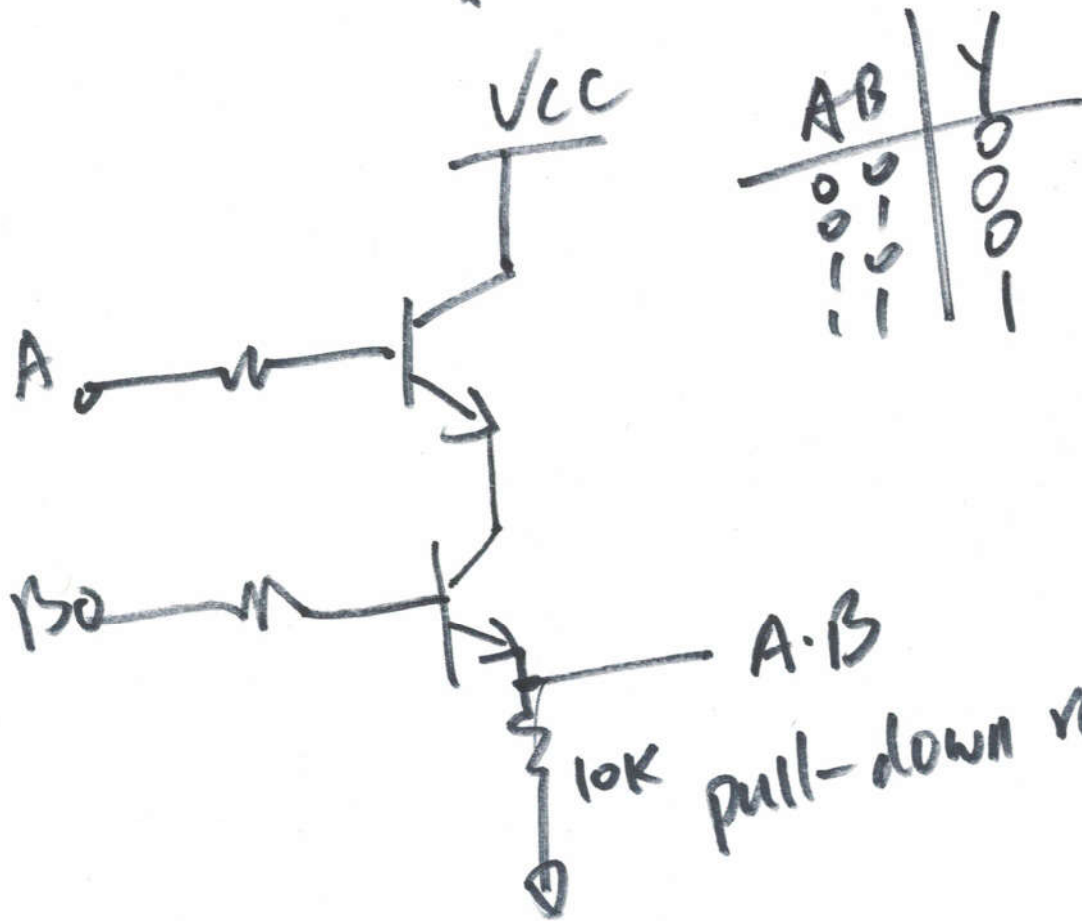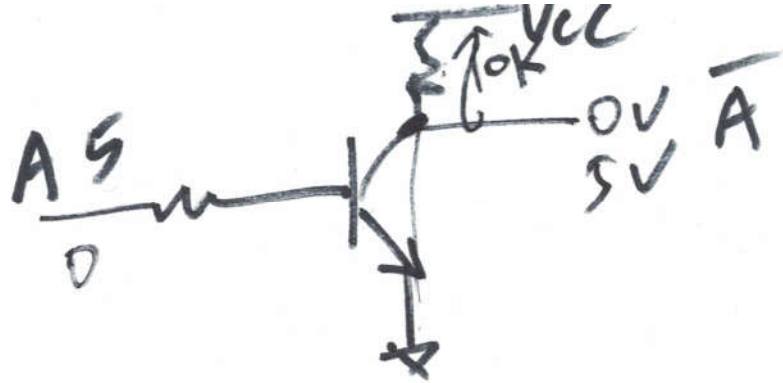

AB	Y
00	0
01	0
10	0
11	1

(4)

Example: NPN BJT,

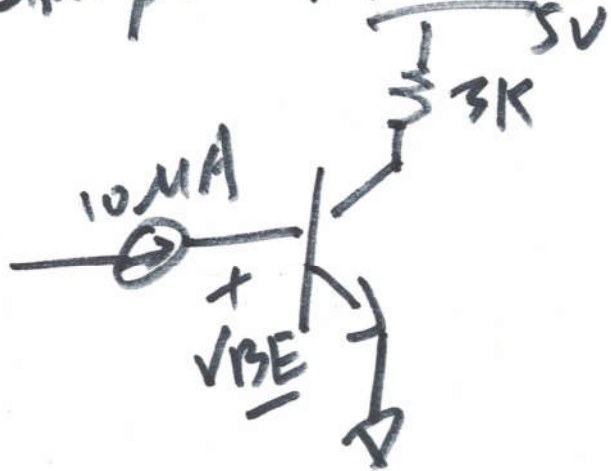

$$I_S = 10^{-15} \text{ A}, \beta = 100$$

① Find V_{BE} and V_{CE} ?

$$I_C = I_S \cdot e^{V_{BE}/V_T}$$

$$V_{BE} = V_T \cdot \ln \frac{I_C}{I_S}$$

$$V_T = 25 \text{ mV}$$

$$I_C = \beta \cdot I_B = 100 \cdot 10 \mu\text{A} = 1 \text{ mA}$$


$$I_S = 10^{-15} \text{ A}$$

$$V_{BE} = 0.69 \text{ V}$$

② Replace the 10 mA current source with a resistor and 5V. R ?

$$V_R = 5 \text{ V} - V_{BE} = 5 - 0.69 = 4.31 \text{ V}$$
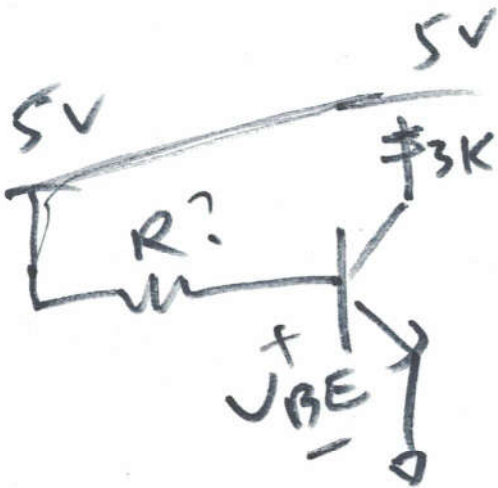
$$R = \frac{V_R}{I_B} = \frac{4.31 \text{ V}}{10 \mu\text{A}} = 431 \text{ k}\Omega$$



⑤

Example: NPN, $V_{BE} = 0.7V$ at $I_C = 1mA$.
 Find V_{BE} at $I_C = 0.1mA$ and $10mA$.

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\begin{cases} I_{C1} = I_S e^{\frac{V_{BE1}}{V_T}} \\ I_{C2} = I_S e^{\frac{V_{BE2}}{V_T}} \end{cases}$$

$$\frac{I_{C1}}{I_{C2}} = \frac{I_S e^{\frac{V_{BE1}}{V_T}}}{I_S e^{\frac{V_{BE2}}{V_T}}}$$

$$\frac{1mA}{0.1mA} = e^{\frac{0.7V - V_{BE2}}{V_T}}$$

$$25mV \leftarrow \frac{V_T}{I} \ln 10 = 0.7V - V_{BE2}$$

$$V_{BE} = 0.64V$$

(b)