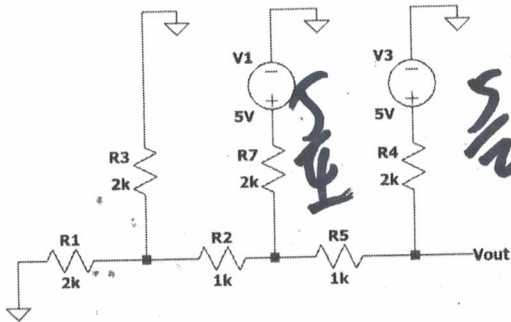



ENGR338 Digital Electronics (55 minutes, close-book, close-notes)

1. Use Thevenin's equivalent theory and superposition to solve for V_{out} in the following circuit (show the calculation process for credits). (25 points)



$1.25 + 2.5 = 3.75V$

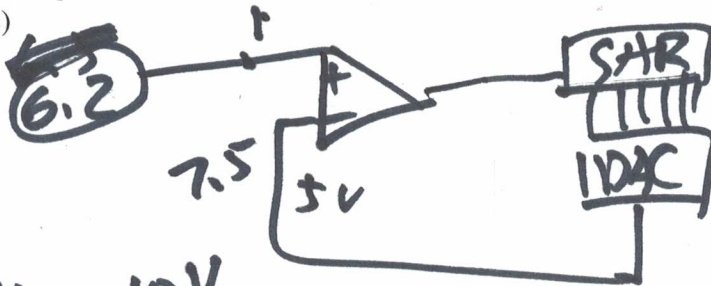
2. For a 5-bit SAR ADC, V_{REF} for the DAC is 10 V, V_{in} at a moment is 6.2V. Show all the states of the ADC's output in a state diagram. Show both the analog voltage and the digital voltage for each state. (25 points)



$1LSB = \frac{10V}{2^5} = \frac{10V}{32} = \dots$



$11000 \cdot \frac{10}{32}$

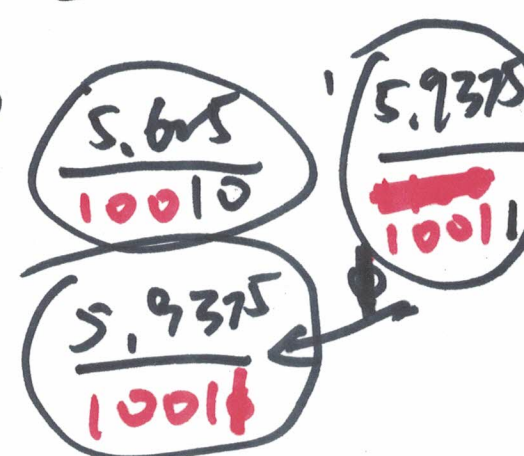




DOEF

3. Convert the following logic expressions to AOI circuits and DESIGN the stick diagram layouts of the following logic circuits. Label the signals at the gates but don't connect the gates with wires (the stick diagram must NOT be broken in the PMOS and NMOS series – one line for all PMOSes and one line for NMOSes). (25 points)

a. $\overline{ABCD} + \overline{CDE} + \overline{AB}$
 b. $\overline{ABC} + \overline{DE(EF + A)}$

$= \overline{AB + CDE}$


$= \overline{ABC + DEF + DEA}$

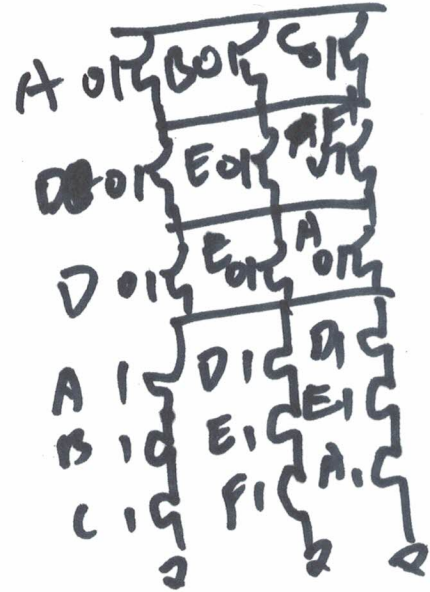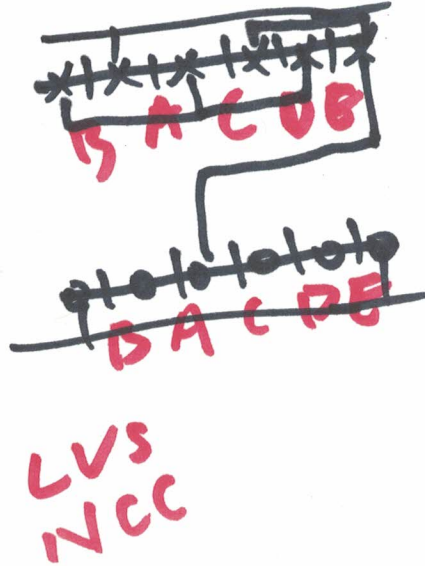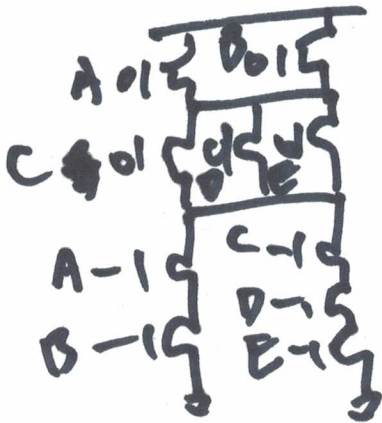


4. Determine the maximum DNL and INL (in LSBs) for a 3-bit DAC (assume V_{REF} is 5 V). What is the ideal resolution of this DAC? (25 points)

Digital Input	Voltage Output
000	0 V
001	0.625 V
010	1.5625 V
011	2.0 V
100	2.5 V
101	3.125 V
110	3.4375 V
111	4.375 V

ideal
 ⋮
 ⋮
 ⋮
 ⋮
 ⋮
 ⋮
 ⋮
 ⋮

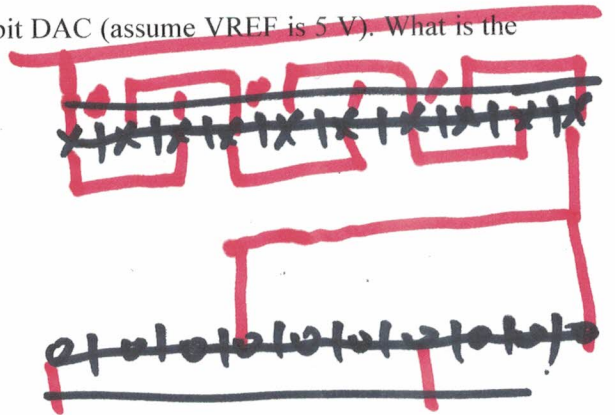

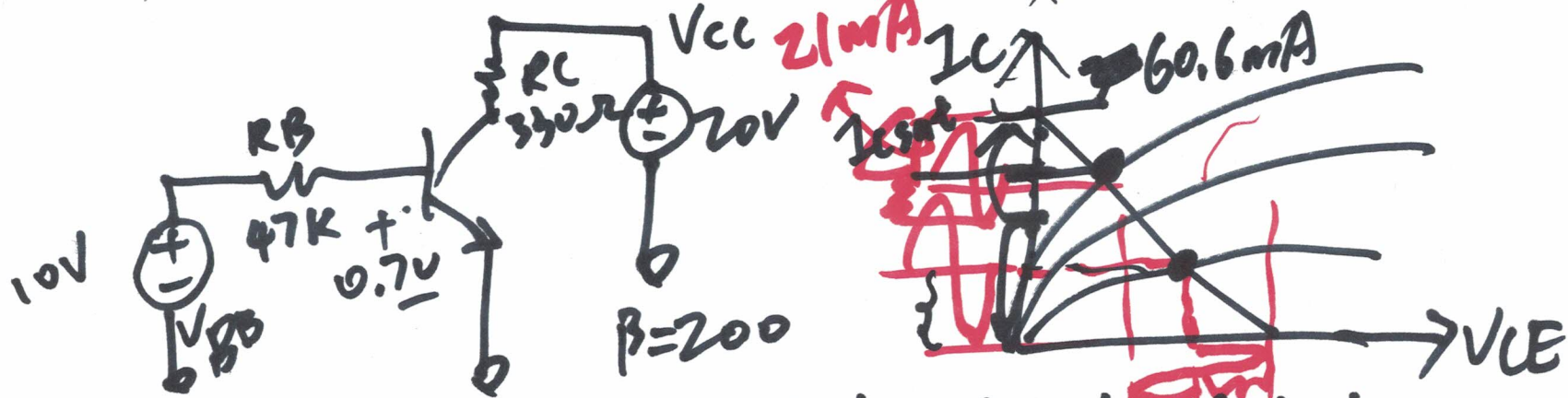

① Determine the Q point and find the peak value of the base current.

The Q-point is defined by I_C and V_{CE}

$$I_B = I_{BQ} = \frac{V_{BE} - V_{BE}}{R_B} = \frac{10 - 0.7}{47K\Omega} = 198 \mu A$$


$$I_C = I_{CQ} = I_{BQ} \cdot \beta = 198 \mu A \cdot 200 = \underline{39.6 mA}$$

$$V_{CE} = V_{CEQ} = V_{CC} - I_C \cdot R_C = 20 - 39.6 mA \times 330\Omega = 6.93 V$$

$$I_{C(sat)} = \frac{V_{CC} - 0}{R_C} = \frac{V_{CE(sat)}}{R_C} = \frac{20V}{330\Omega} = 60.6 mA$$

$$I_{C(sat)} - I_{CQ} = 60.6 mA - 39.6 mA = 21 mA$$

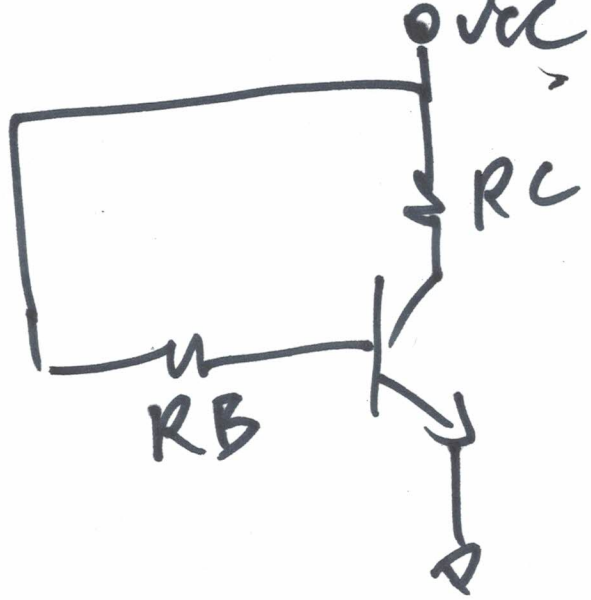The maximum swing range for I_B is $\frac{21 mA}{\beta} = \frac{21 mA}{200} = 105 \mu A$



\Rightarrow You can calculate for the Q-point

Draw the load line

