

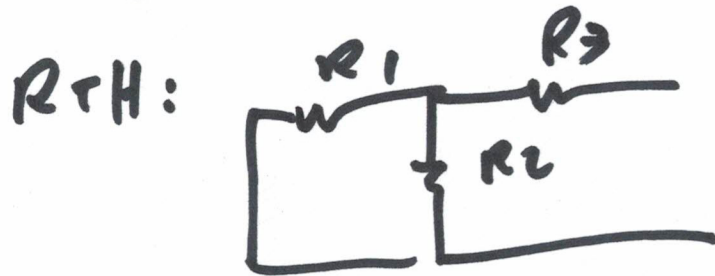
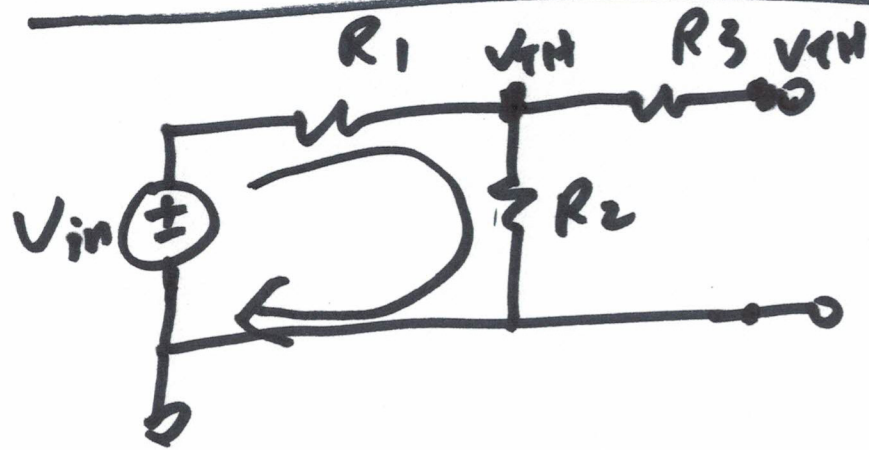


Thevenin's equivalent circuit

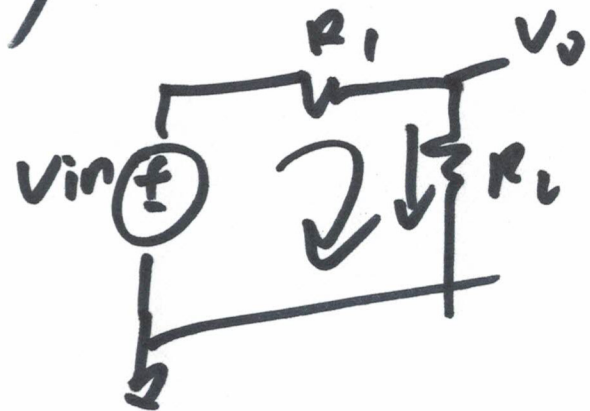


$$R_3 + (R_1 \parallel R_2)$$
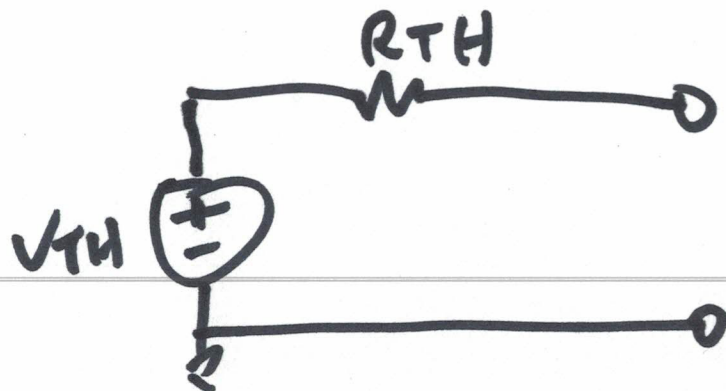
$$V_{TH}: V_{TH} = V_{in} \frac{R_2}{R_1 + R_2}$$



$$\frac{V_0}{V_{in}} = \frac{I \cdot R_2}{I \cdot (R_1 + R_2)}$$


$$V_0 = V_{in} \frac{R_2}{R_1 + R_2}$$

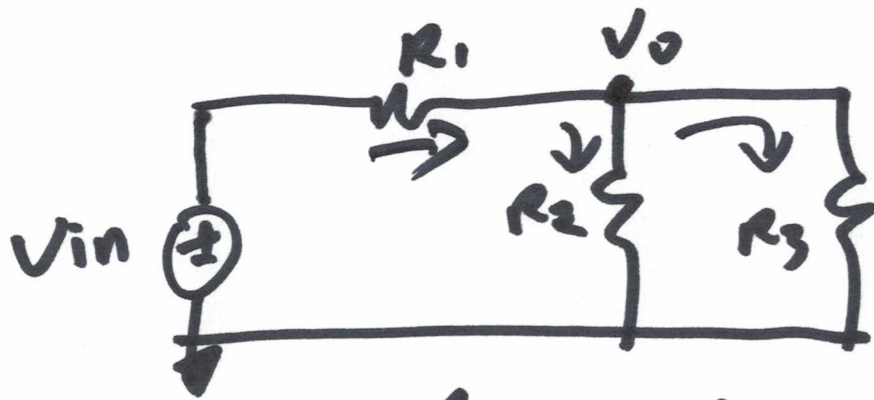


$$V_o = V_{in} \cdot \frac{R_2}{R_1 + R_2} \quad \times$$




SPICE

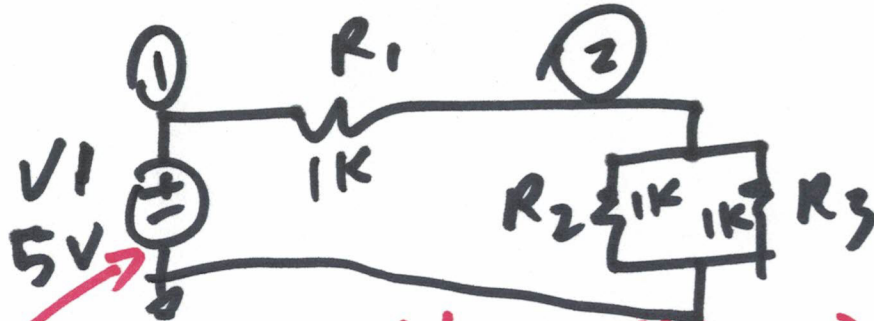

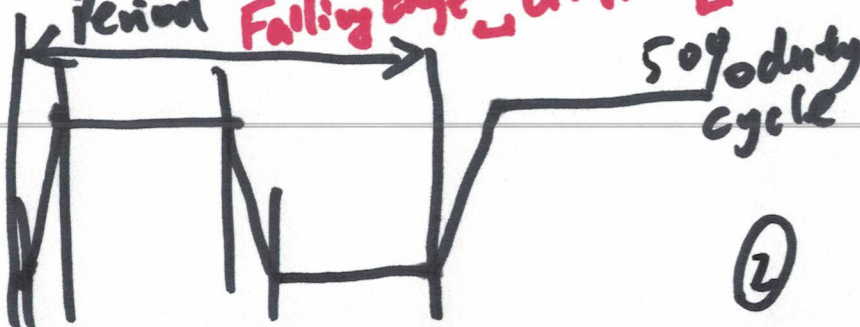
PULSE (0.5 delay risingEdge)
 FallingEdge on time Period



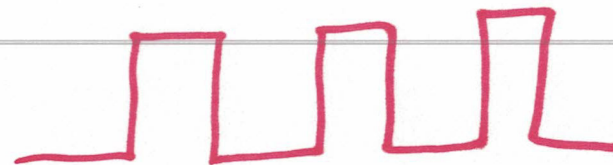
```
V1 1 0 5V
R1 1 2 1K
R2 2 0 1K
R3 2 0 1K
.tran 0! 0.001
```



Super position

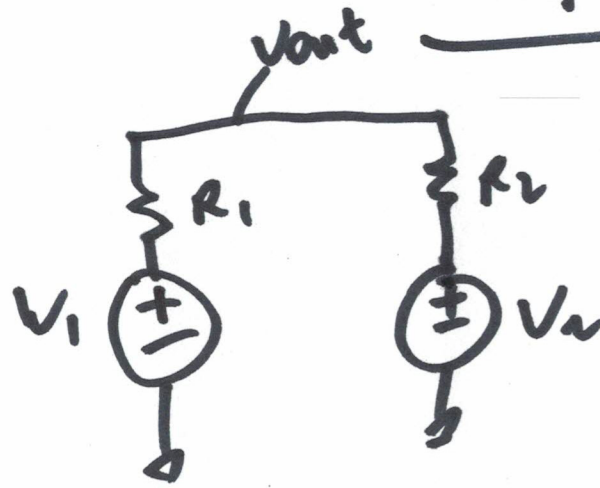


V_1 only:

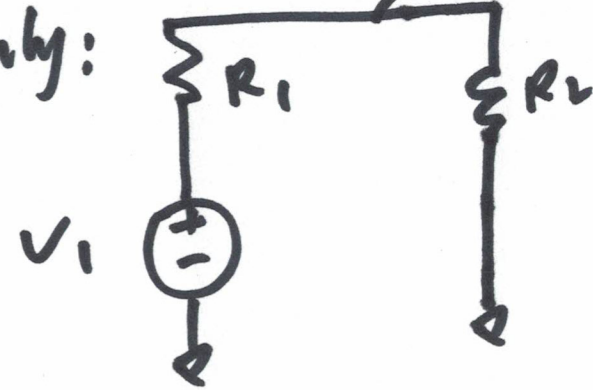

$$V_{01} = V_1 \cdot \frac{R_2}{R_1 + R_2}$$



V_2 only:

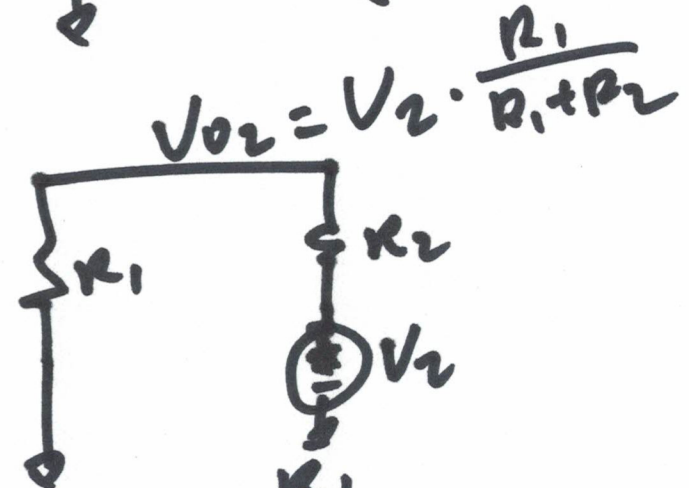

$$V_{02} = V_2 \cdot \frac{R_1}{R_1 + R_2}$$

$$V_0 = V_{01} + V_{02} = V_1 \cdot \frac{R_2}{R_1 + R_2} + V_2 \cdot \frac{R_1}{R_1 + R_2}$$

DAL

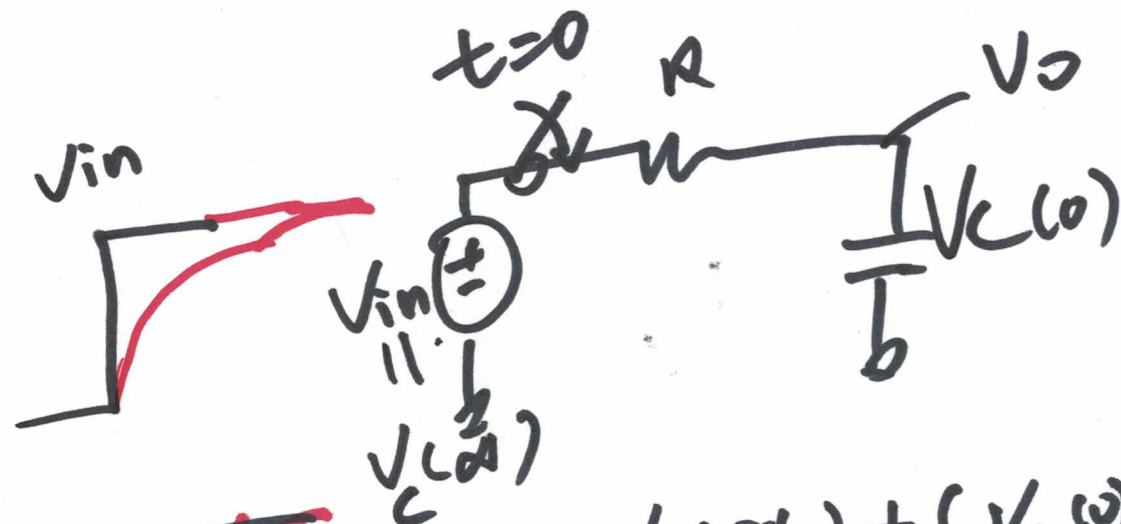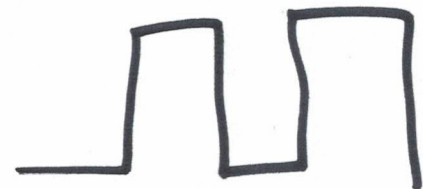


$$v_c(t) = v_c(\infty) + (v_c(0) - v_c(\infty))e^{-t/RC}$$

I: $v_c(0) \neq 0$

II: $v_c(0) = 0$, $v_c(t) = v_c(\infty) - v_c(\infty) \cdot e^{-t/RC}$

$= v_c(\infty)(1 - e^{-t/RC})$

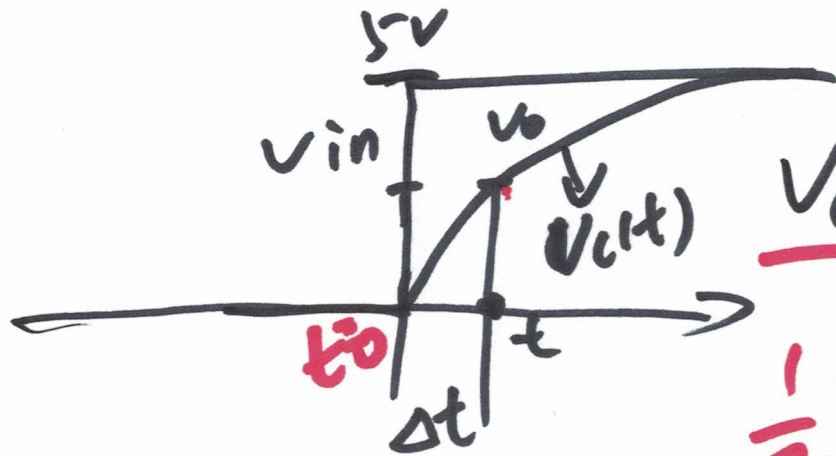

$$\underline{V_C(t)} = \underline{V_C(\infty)} (1 - e^{-t/RC})$$

$$\frac{1}{2} V_C(\infty) = V_C(\infty) (1 - e^{-t/RC})$$

$$e^{-t/RC} = 0.5$$

$$\ln e^{-t/RC} = \underline{\underline{\ln 0.5}}$$

$$\frac{-t}{RC} = -0.7$$

$$\boxed{t = 0.7RC}$$