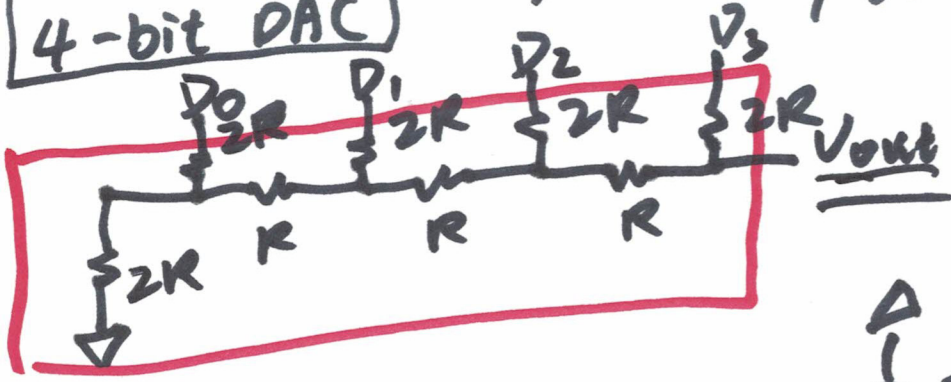


(5V)

4-bit DAC


R-2R DAC

$D_0 - D_3$



$D_3 D_2 D_1 D_0$
↑
MSB
↓
LSB
1111


D_3 only:

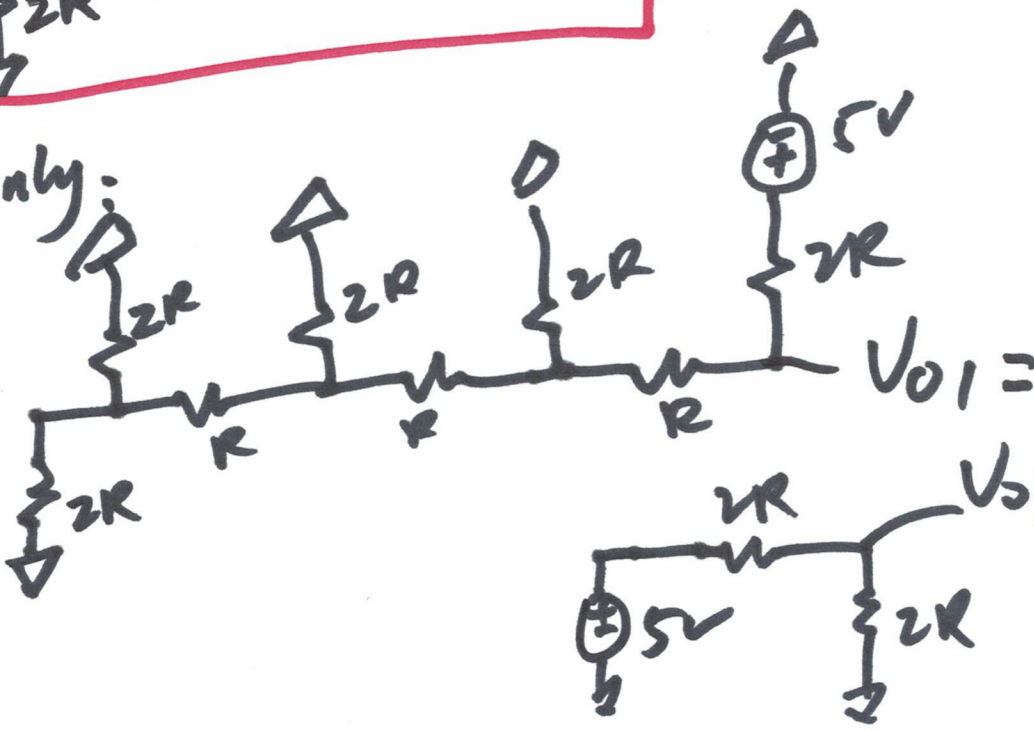



$$V_{01} = \frac{5}{2} V = 2.5V$$





①

D_2 only:

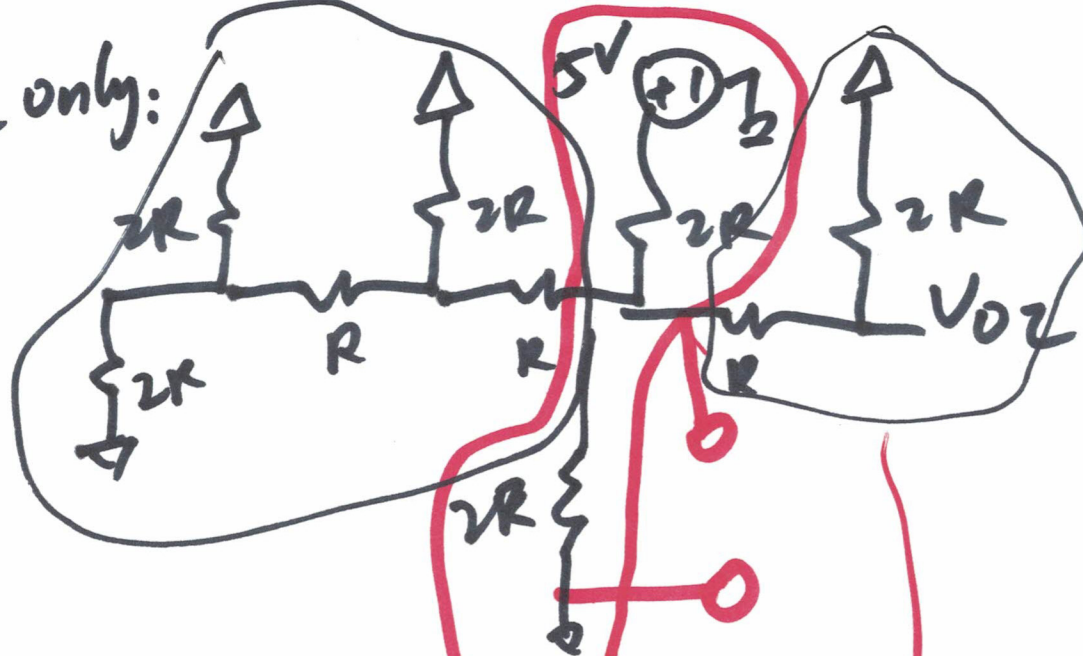


0/00

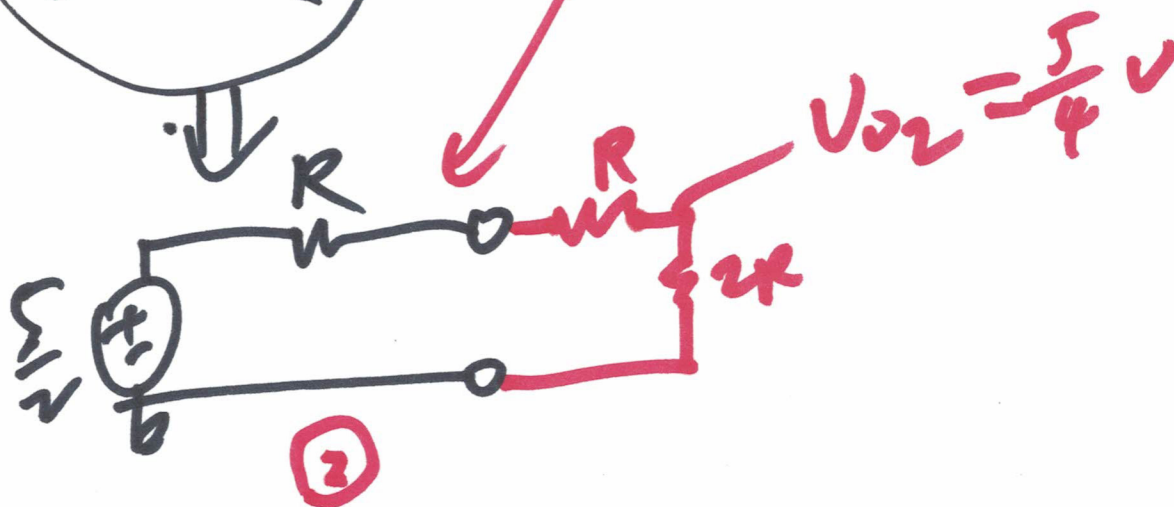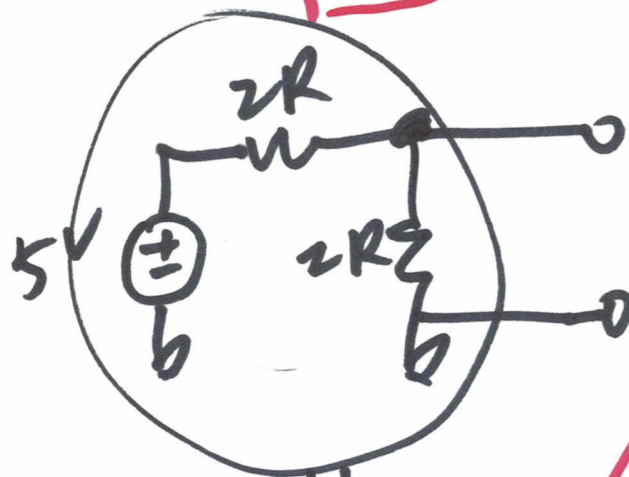


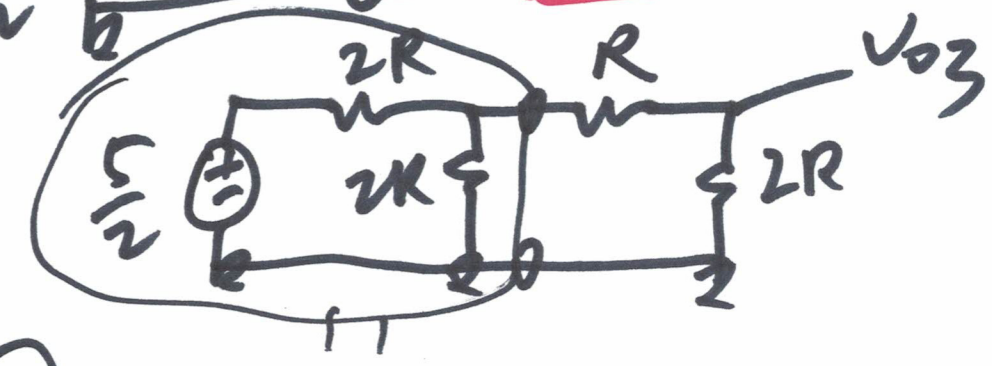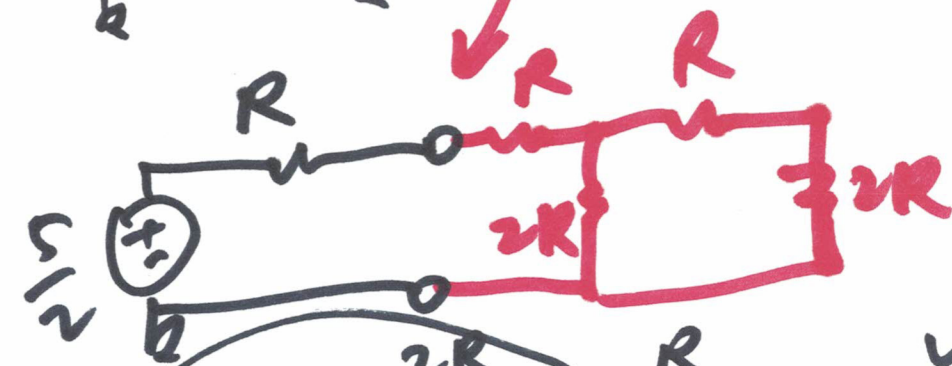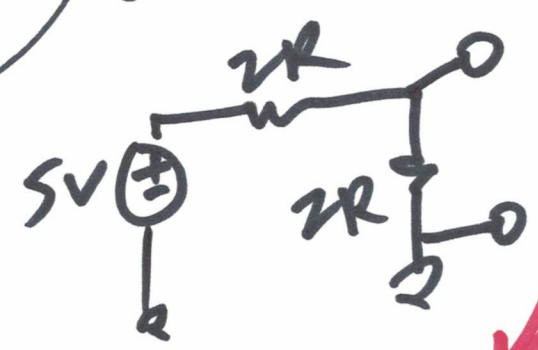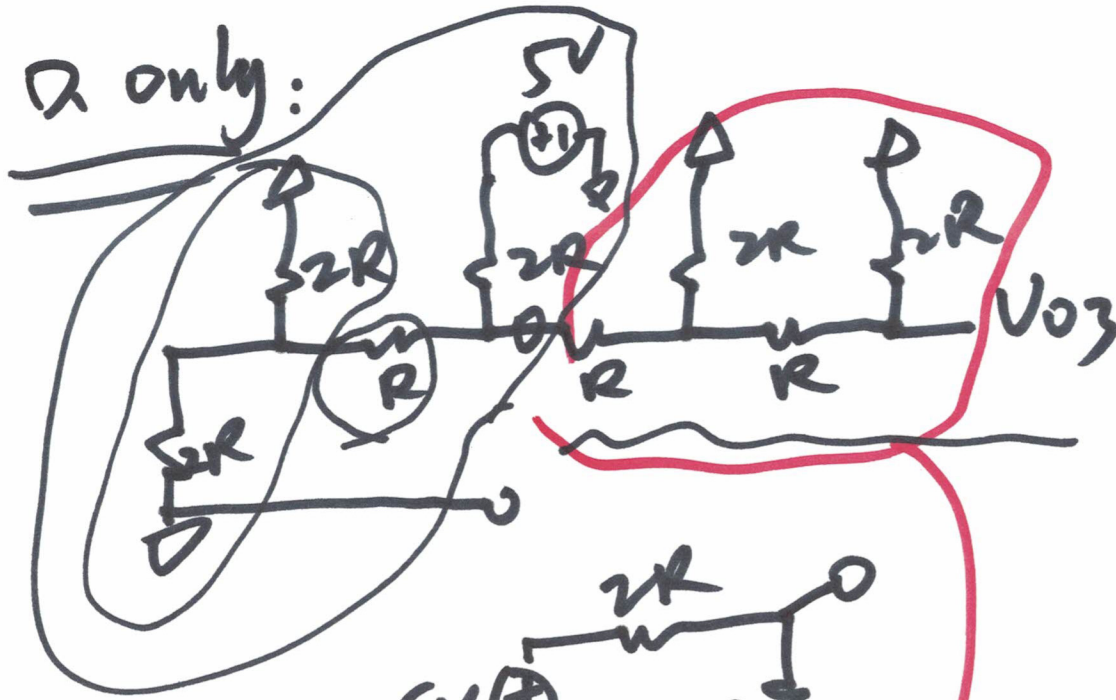

(4)

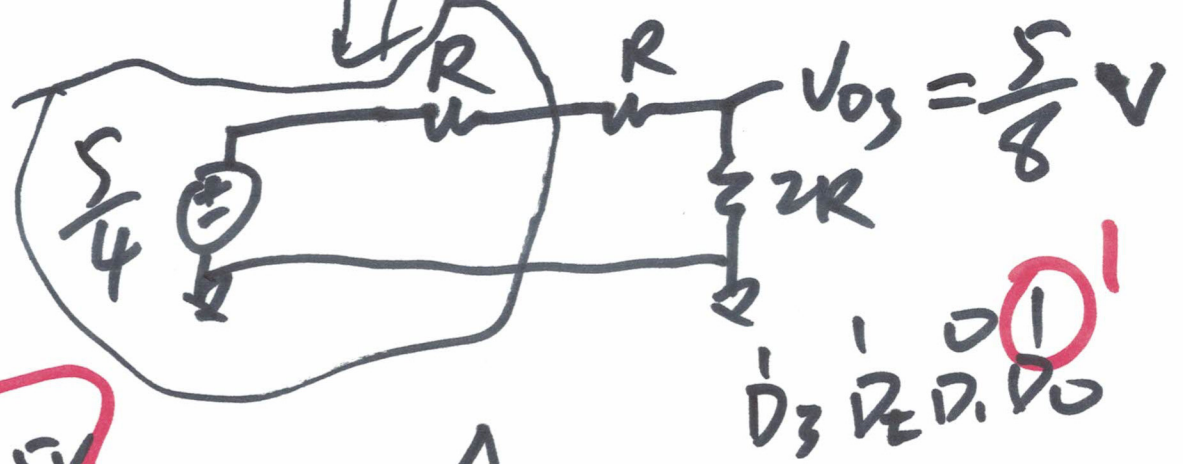

D_0 only:

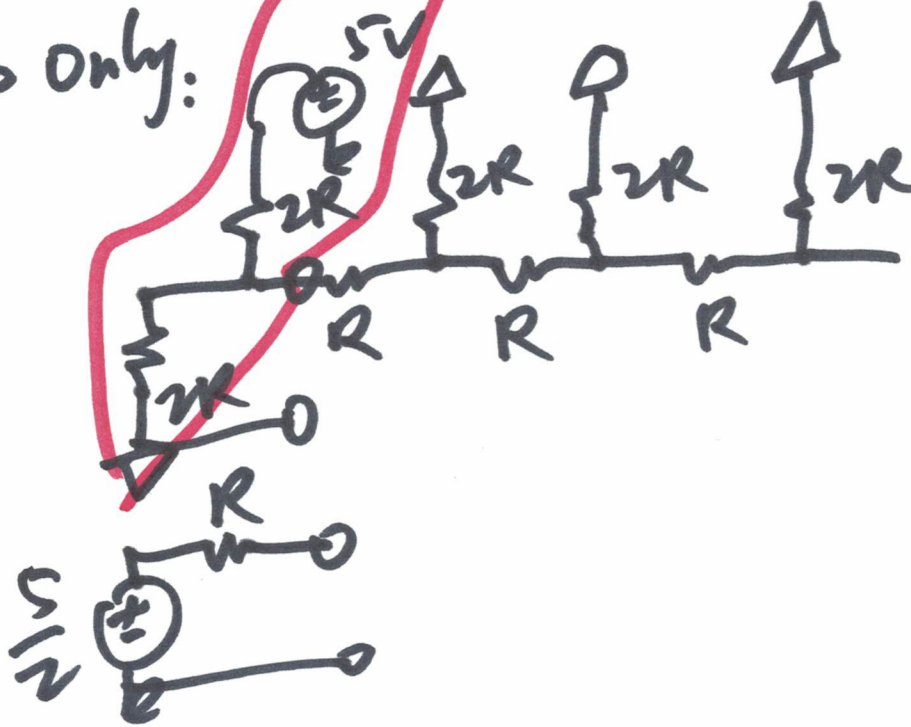

$V_{04} = \frac{5}{16}$ V
 1.5 bits resolution
 $\frac{5}{20}$ V


$$\frac{5}{32} \checkmark$$

(5)

A/D C → Analog to Digital Converter

LSB: Least Significant Bit


MSB: Most

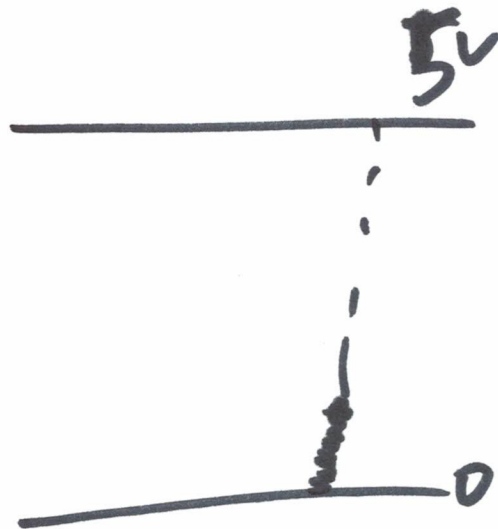

10-bit

$$\frac{5V}{2^{10}} = 4.8mV$$

1mV

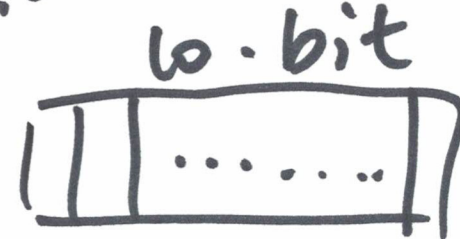


$$2^{10} = 1024$$

$$\frac{5V}{2048} = 2.5mV$$

13-bit

(b)

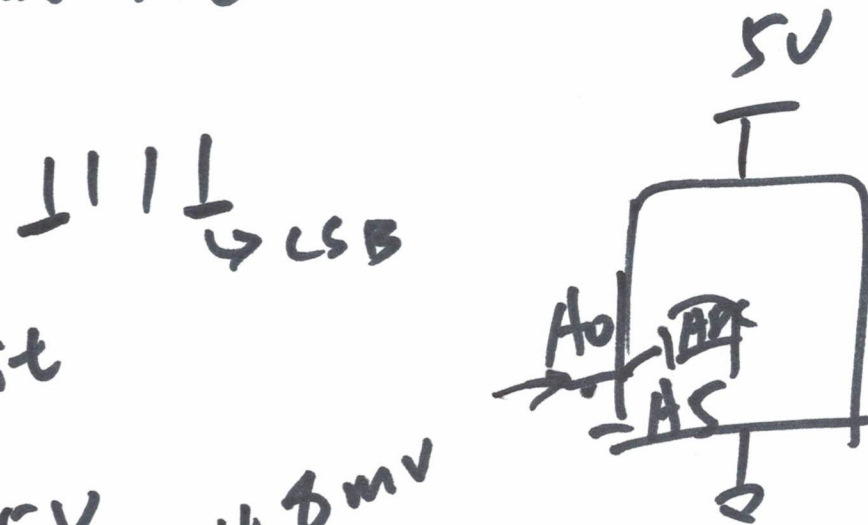

0-5V reference
1mV change sensitivity required.
resolution of ADC to be used?

$$\frac{5}{2^x} = \frac{5V}{1mV} = \frac{2^x}{1453}$$

$$x = \log_2 \frac{5V}{1mV}$$

$$= \log_2 5000 = 12.288$$

$\Rightarrow 13$

(7)

DAC full-scale value V_{FS}

DAC input: 1111 + 1 = 10000

$$V_{out} = \frac{5}{16} + \frac{5}{8} + \frac{5}{4} + \frac{5}{2}$$

$$= \frac{5}{16} + \frac{10}{16} + \frac{20}{16} + \frac{40}{16}$$

$$= \frac{75}{16} = \boxed{} \frac{80}{16} = 5V$$

(18)