

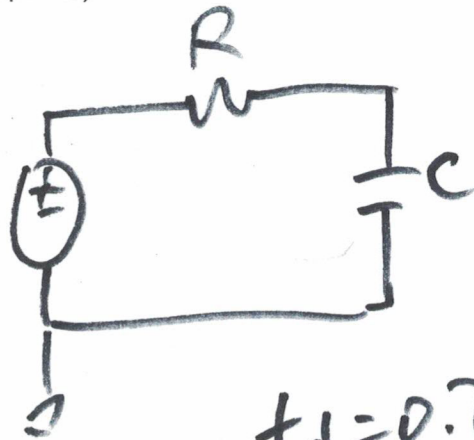


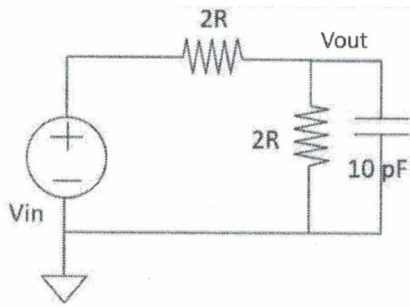1. $R = 10k$, determine time delay at V_{out} . (15 points)



$$t_d = 0.7RC$$

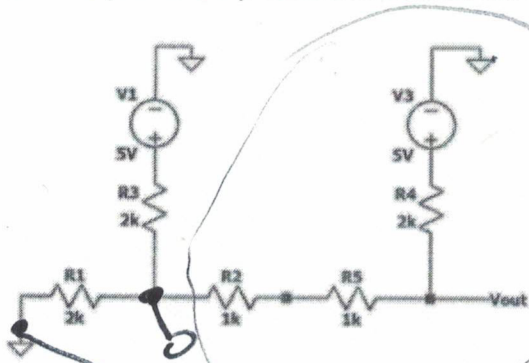
2. Use Thevenin's equivalent theory and superposition to solve for V_{out} in the following circuit (show the process/equivalent circuits for full credit). (15 points)





$$V_1 = 2.5V \cdot \frac{2k}{5k} = 1V$$

$$V_2 = 5V \cdot \frac{3k}{5k} = 3V$$


$$V_{out} = V_1 + V_2 = 4V$$

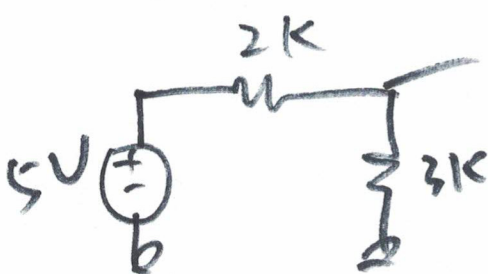

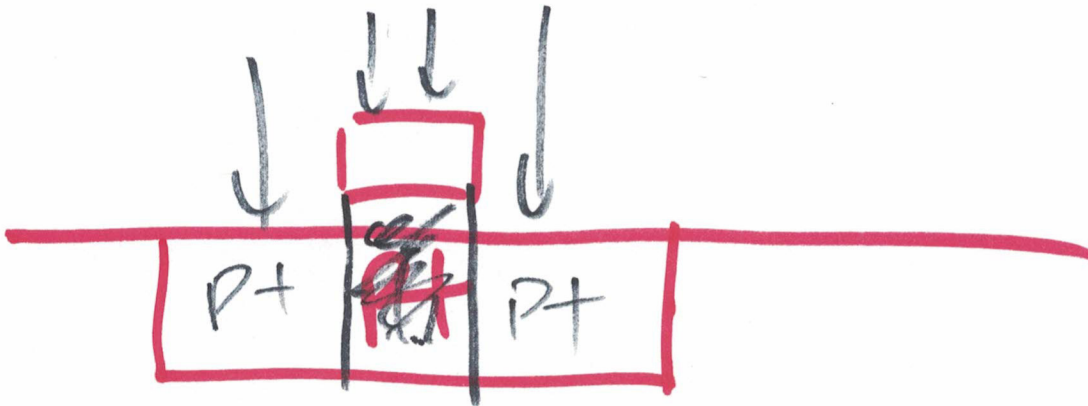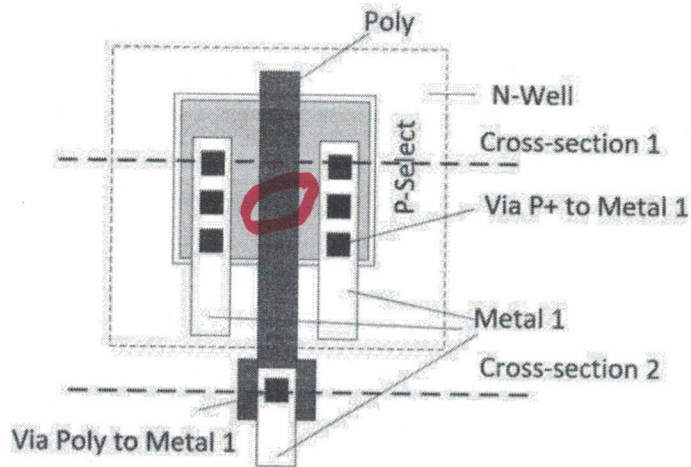
3. The following figure shows the top-view of a layout. Draw the cross-sectional views (cross-section 1 and cross-section 2 of the locations indicated by the dashed lines. (15 points)



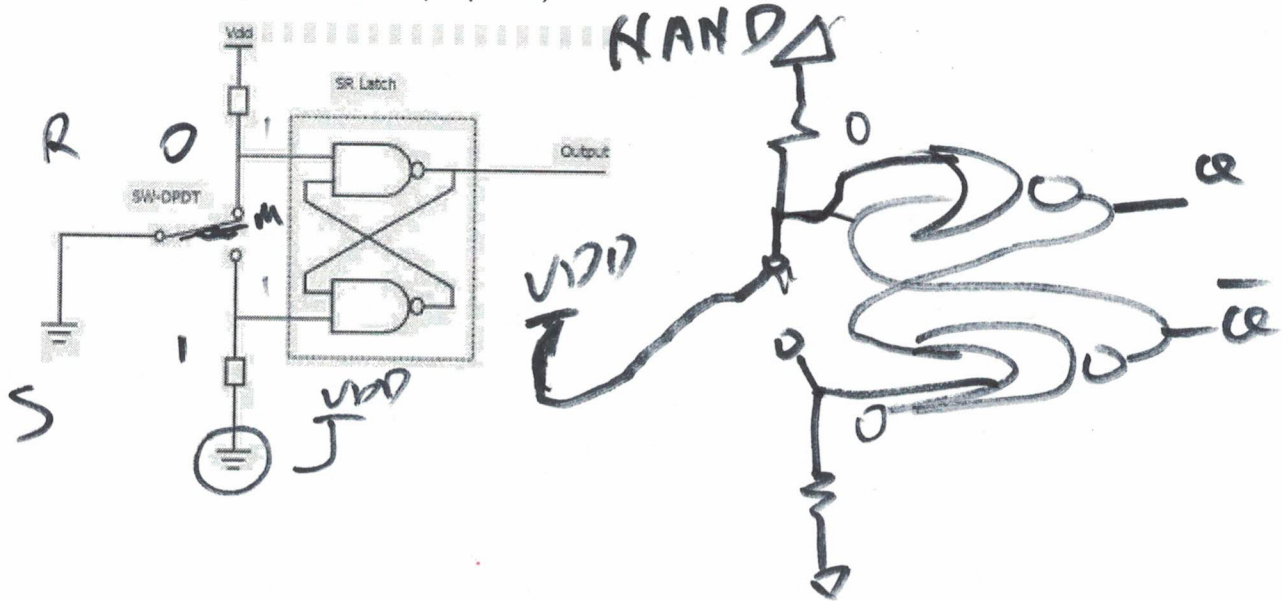
4. A debounce circuit is an electronic circuit that eliminates false switching signals caused by the mechanical bouncing of switch contacts, providing a clean, single output signal to a digital circuit. Would the following circuit serve as a debounce circuit? Why or why not? If it wouldn't, how to fix it? What are the typical resistor values of the two resistors? Design a debounce circuit that uses NOR gates instead. (15 points)



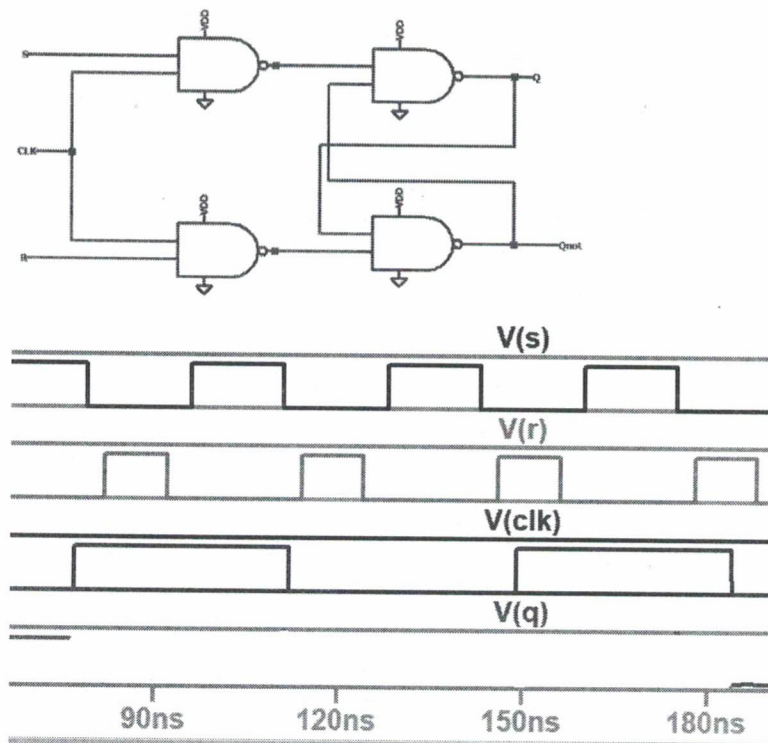5. Complete the following waveforms of the DFF output $V(q)$. (15 points)



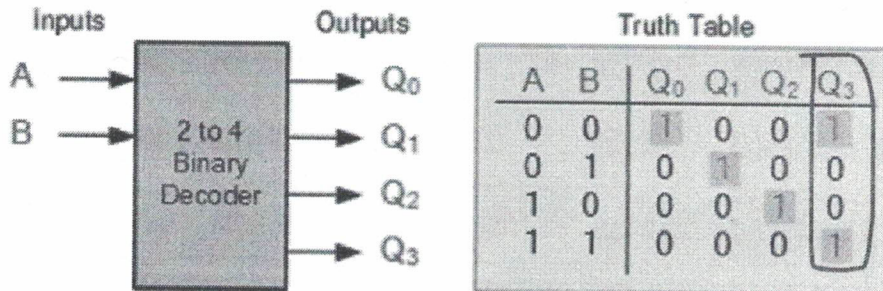
6. Find the AOI schematic and the stick diagram of output Q3 for the following decoder. Note that the signal input is A and B, output is Q3. If A_not or B_not signals are needed, you need inverters to invert A and B. The stick diagram should include all circuits between the power and GND rails. Gates should be labeled and aligned. (25 points)



$$Q_3 = \bar{A}\bar{B} + AB$$



$$XOR = \overline{A \oplus B}$$

$$= \bar{A}B + A\bar{B}$$

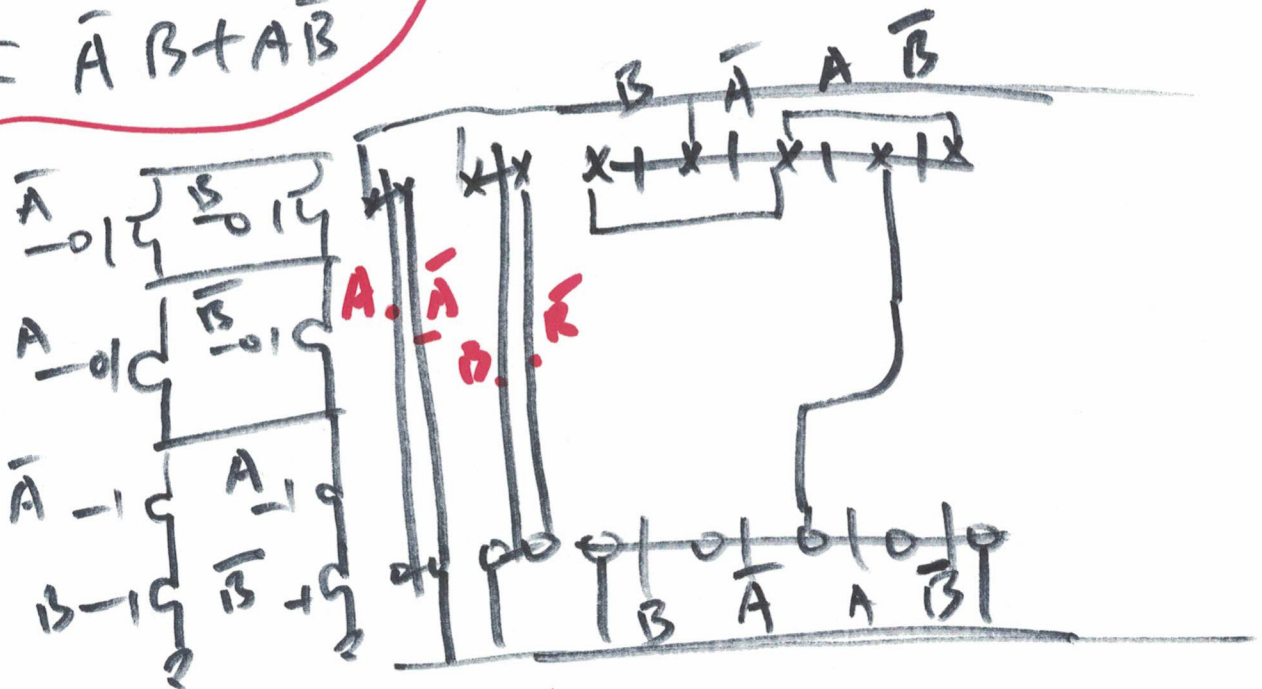


The charge Pump


① Voltage Doubler

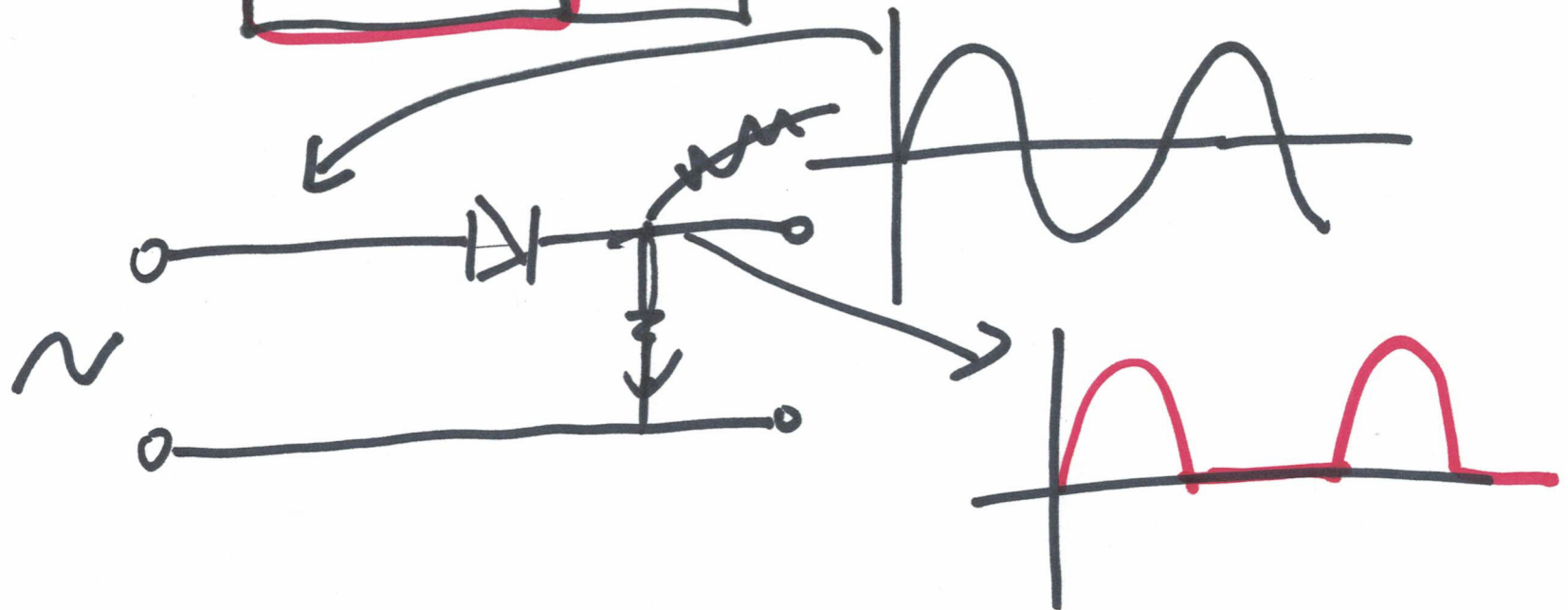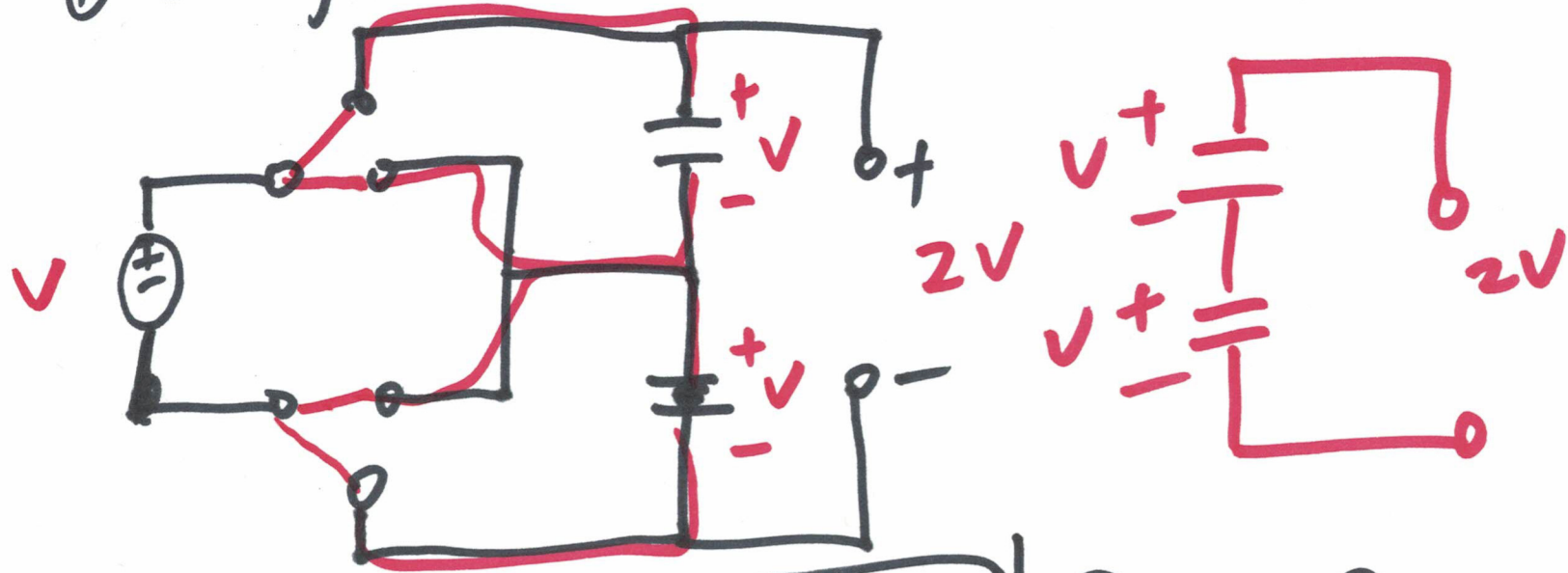



①

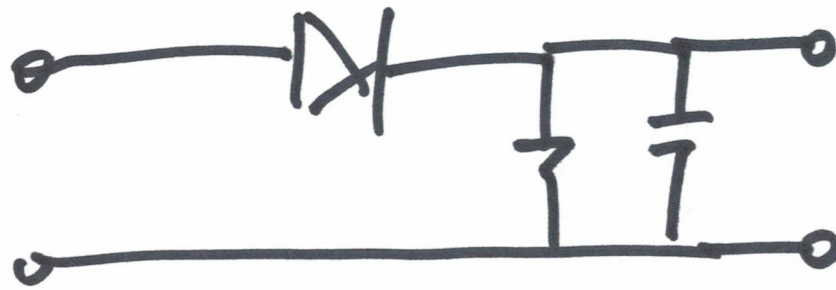

~~the~~ half-wave
rectifier

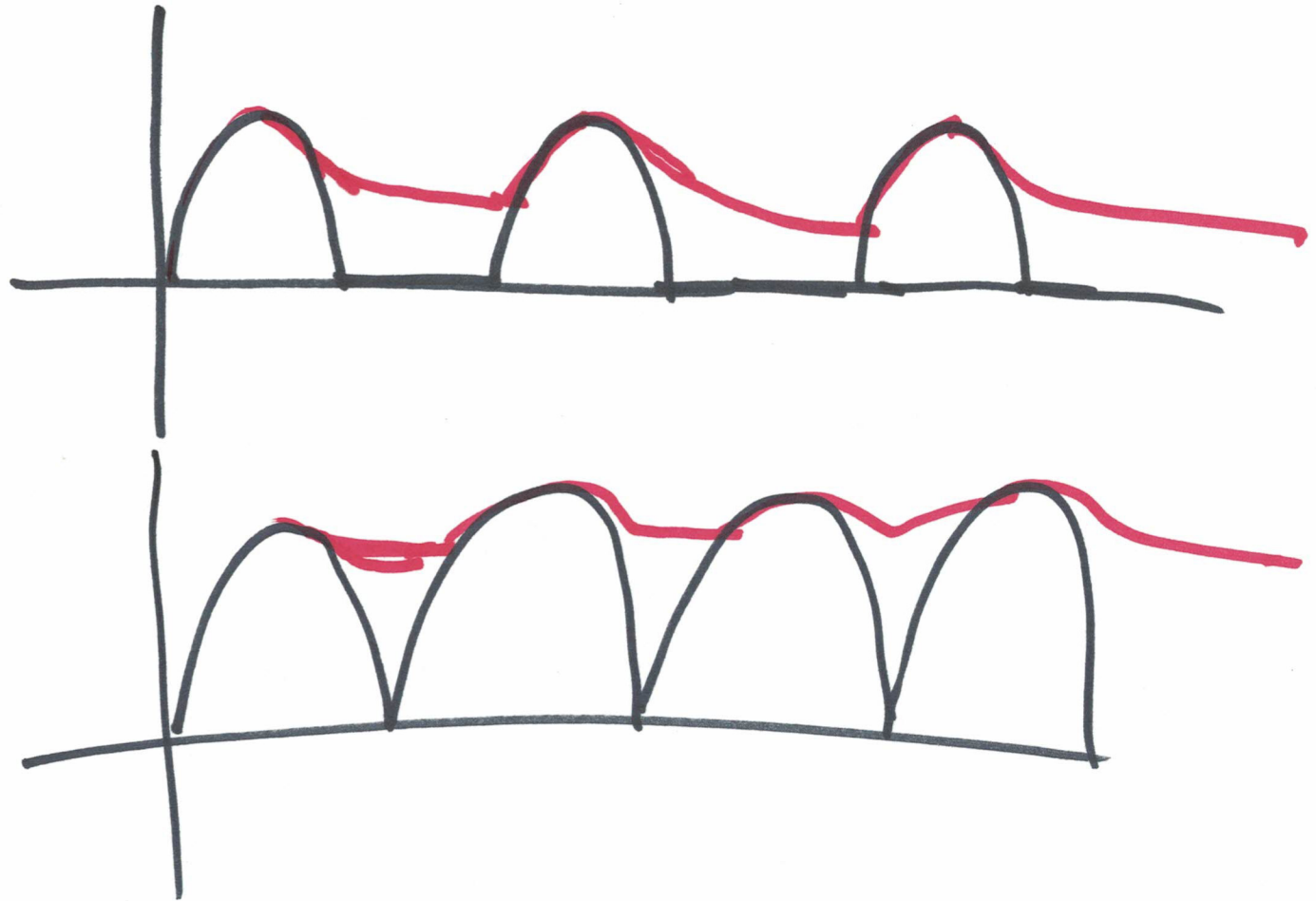


②

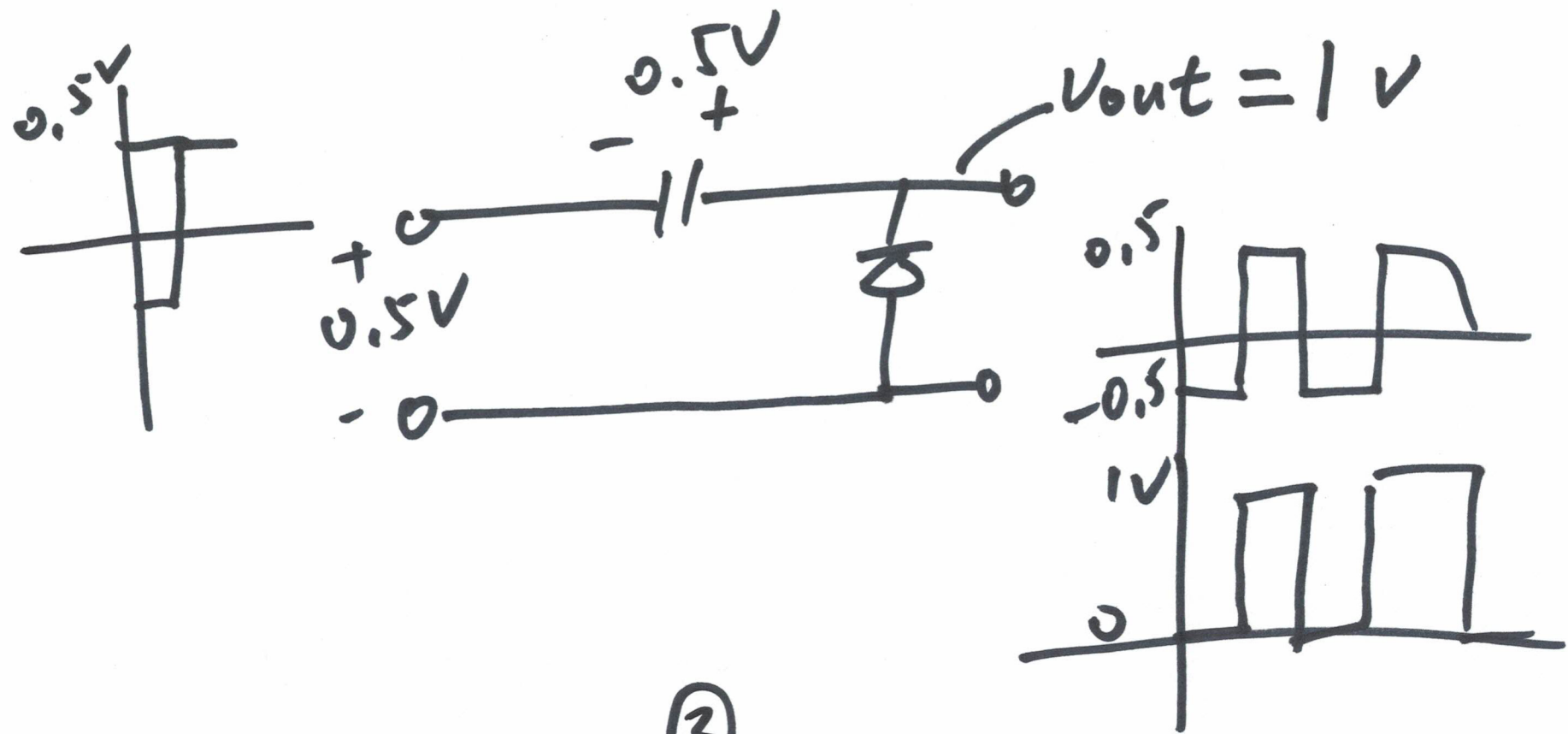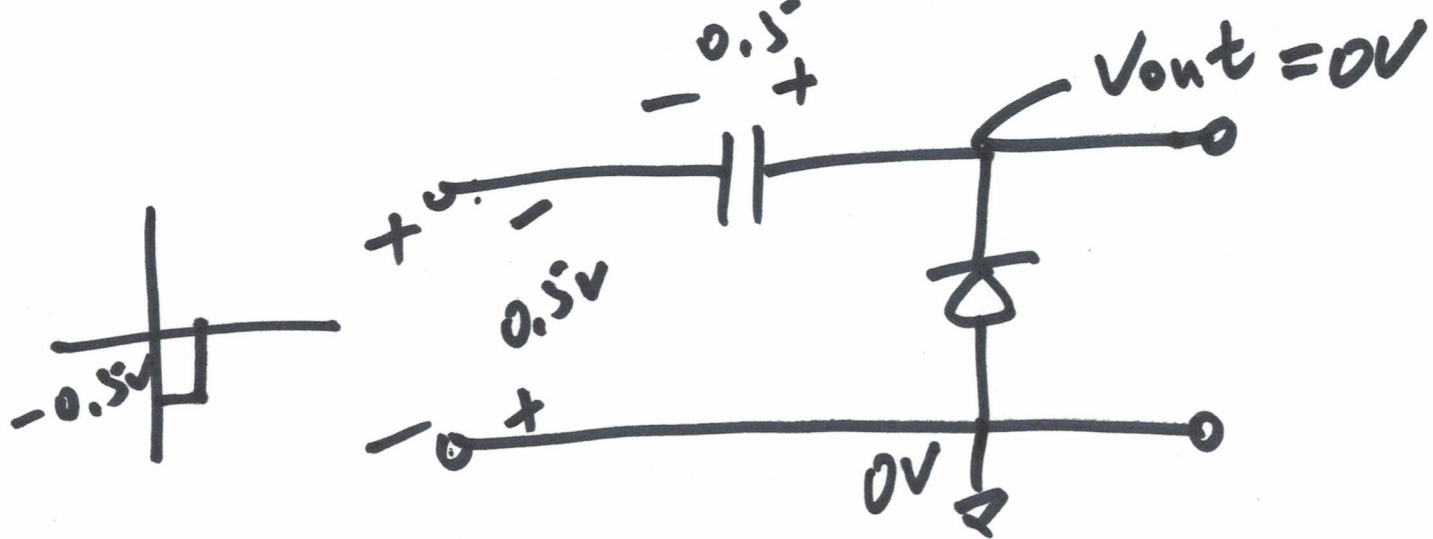


③

charge pump

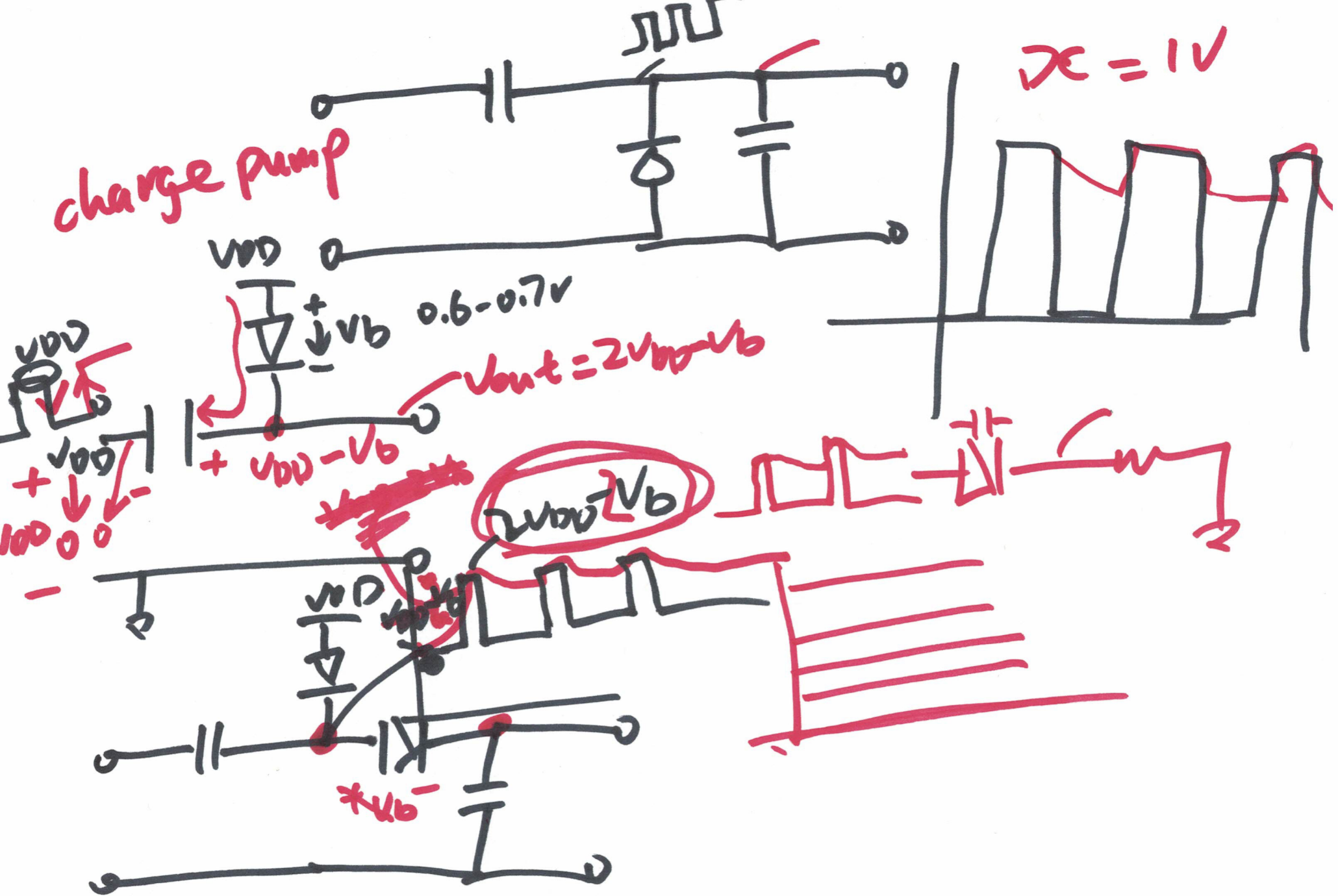

(+)

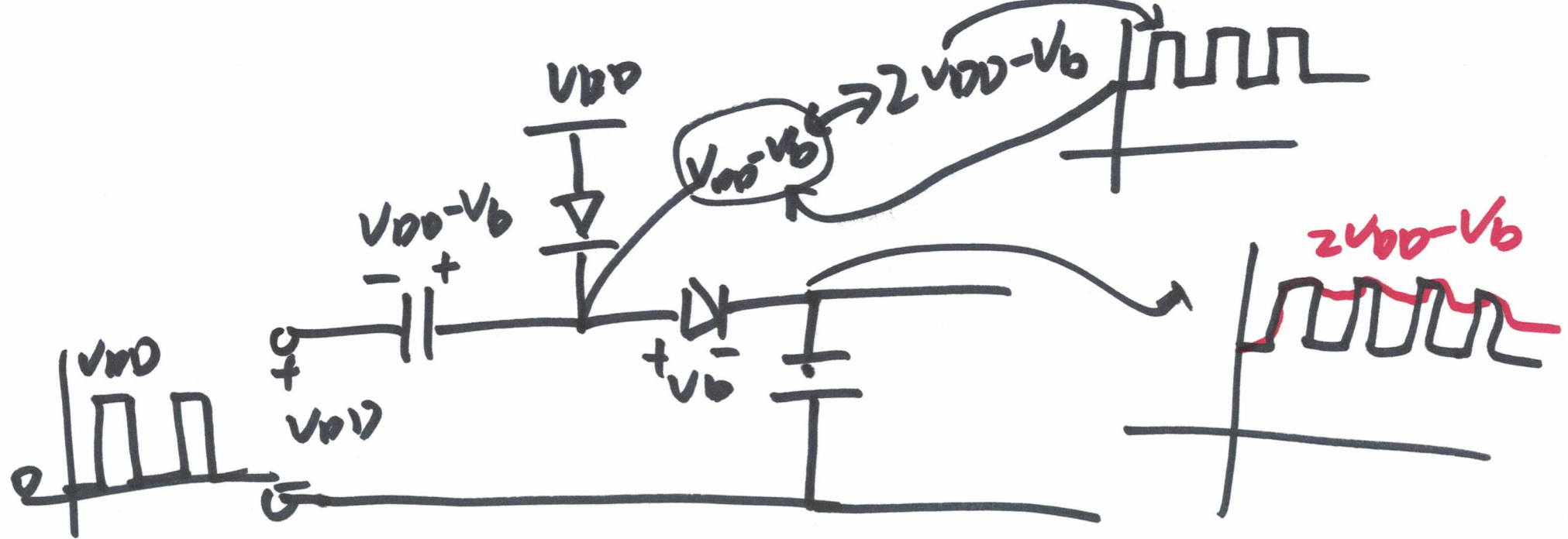

⑤