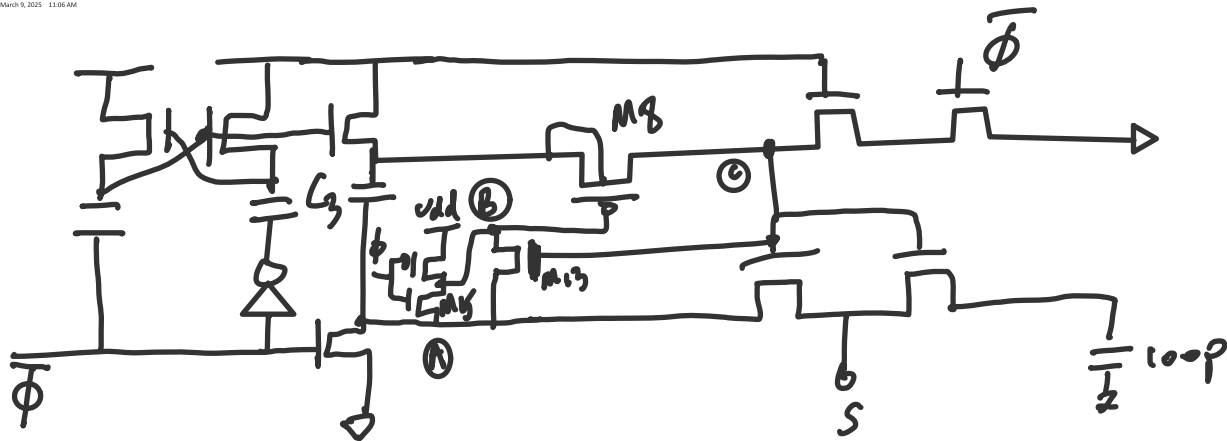




✓ $\bar{\phi} = 1$, reset, hold


✓ $\bar{\phi} = 0$, sample/track



✓ $\phi = 1$, (A) shorted to (B), V_{dd} across C_3 is applied to V_{SG} of M_8 . M_8 is on

✓ S not pushed into C_3 , $V_{C_3} = V_{SG_{M_8}} = V_{dd} + V_S - V_S = V_{dd}$
constant V_{SG} for M_8

✓ M_8 passes the entire $V_{dd} + V_S$ to (C)

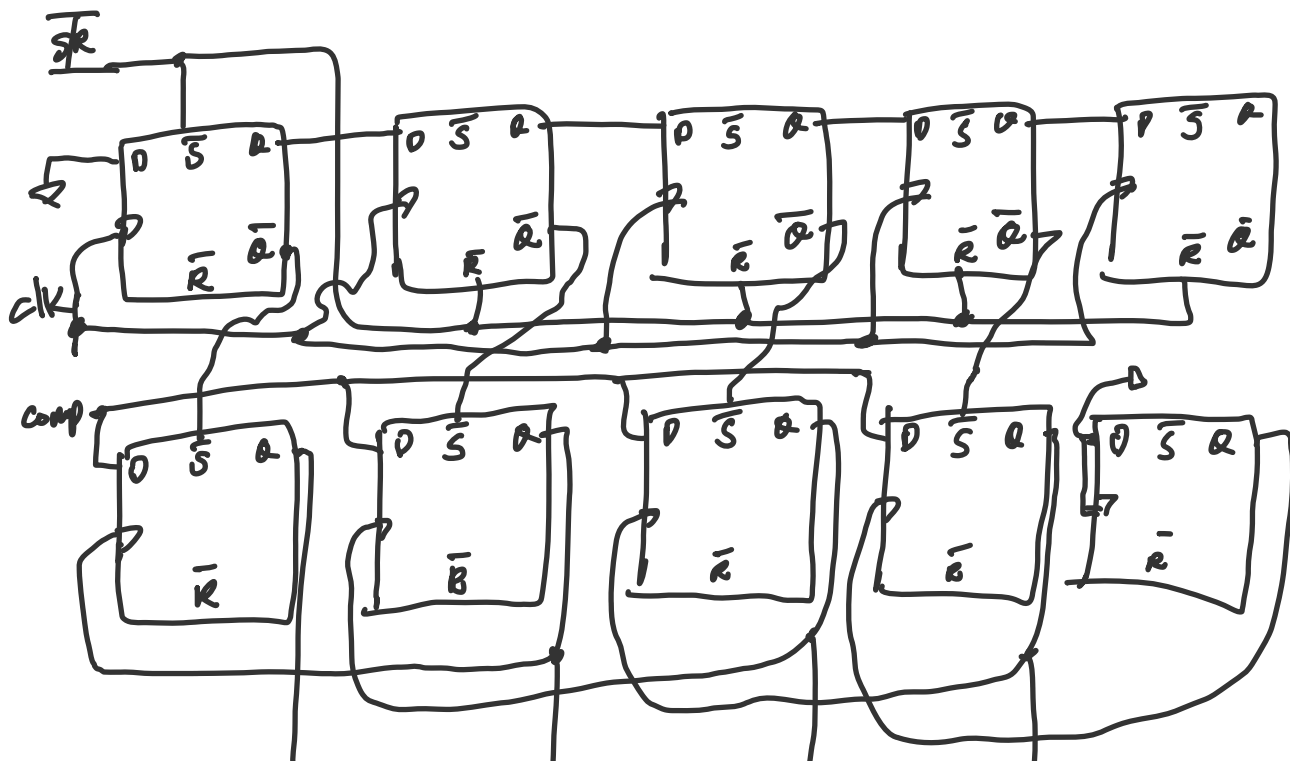✓ when V_S exceeds $V_{dd} - V_{thN}$, M_5 is off. Adding M_{13} there can keep V_G of M_8 to be V_S in this situation.



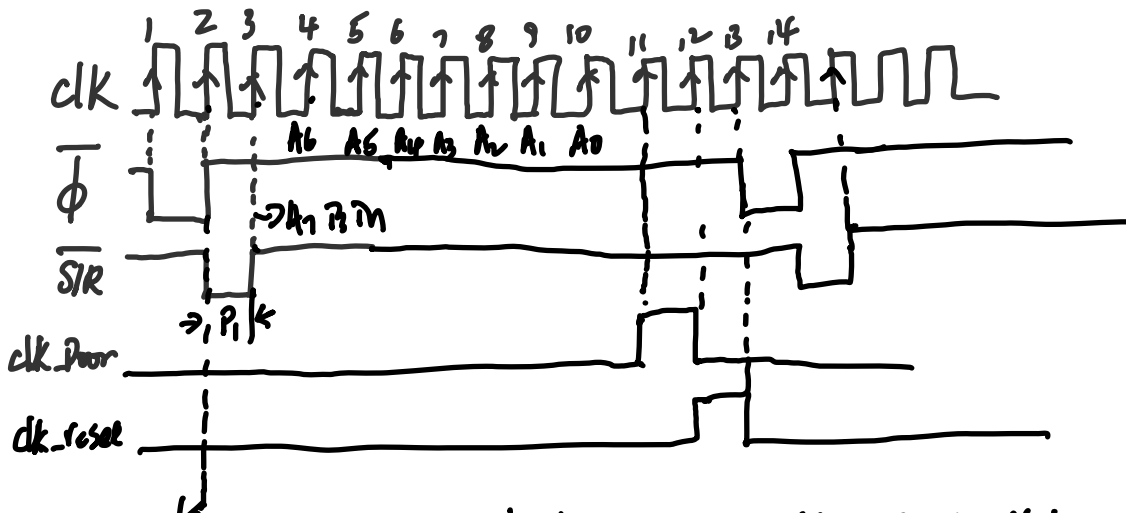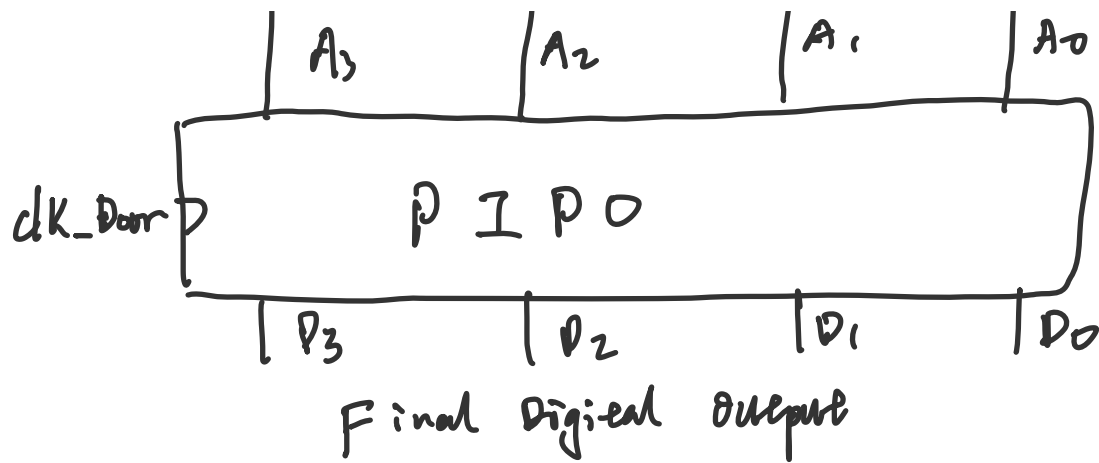

- ✓ Φ back to 1, S/H starts holding, $\overline{S/R}$ resets, SAR outputs 1000...
- ✓ P_1 gives ADC the time to output A_1 , rising edge 3 latches A_1 in by sending a '1' to the first DPP's clk.