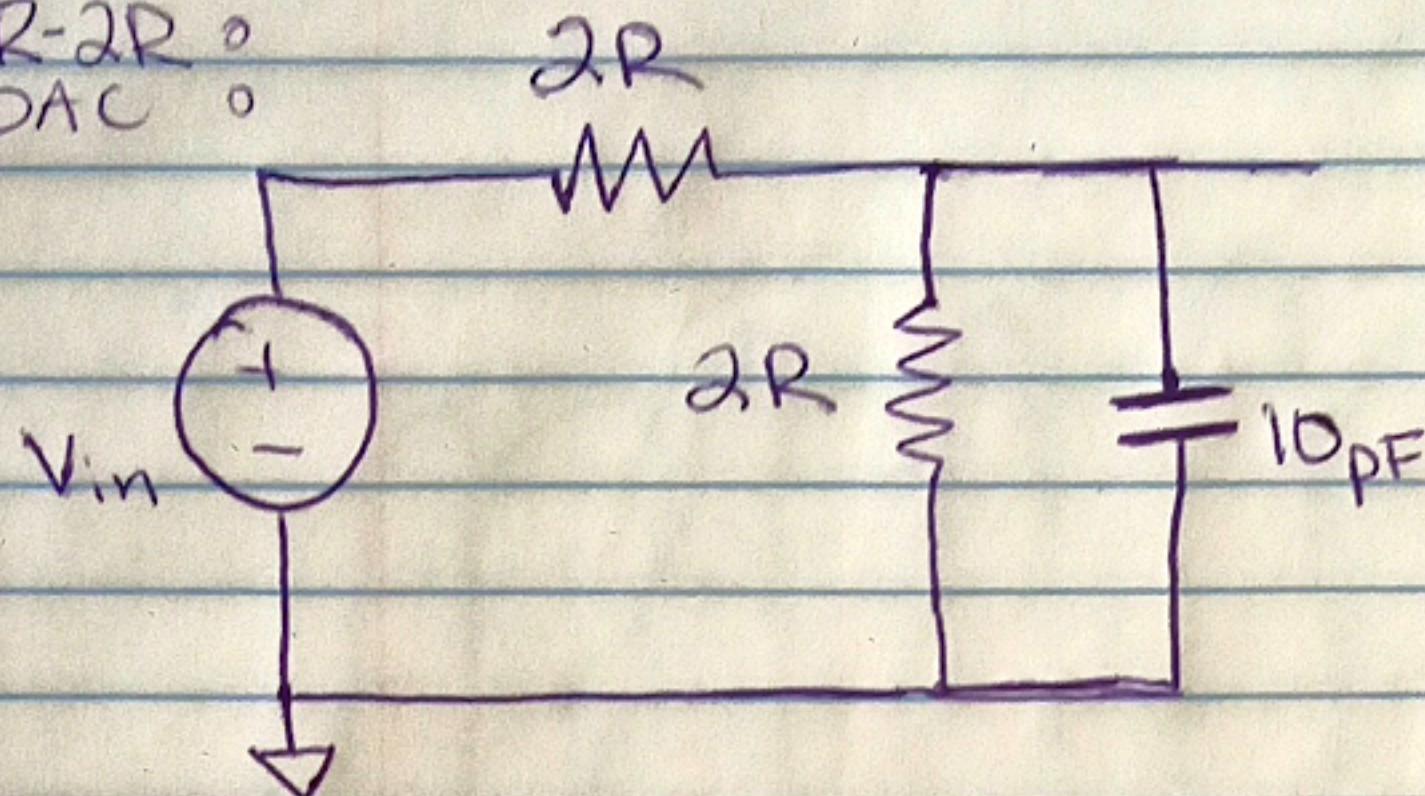



Lab 2 - Task 3

Time Delay of the circuit

R-2R^o
DAC^o



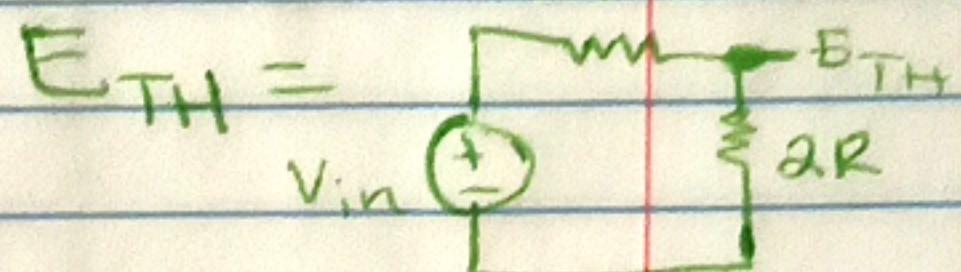
$$R_{TH} = \frac{2R \parallel 2R}{4R} = \frac{2R \cdot 2R}{4R} = R$$



$$V_{in} \left(\frac{2R}{4R} \right) = V_{in} \left(\frac{1}{2} \right)$$

$$= \frac{V_{in}}{2}$$

Thevenin's
Equivalent^o
circuit^o

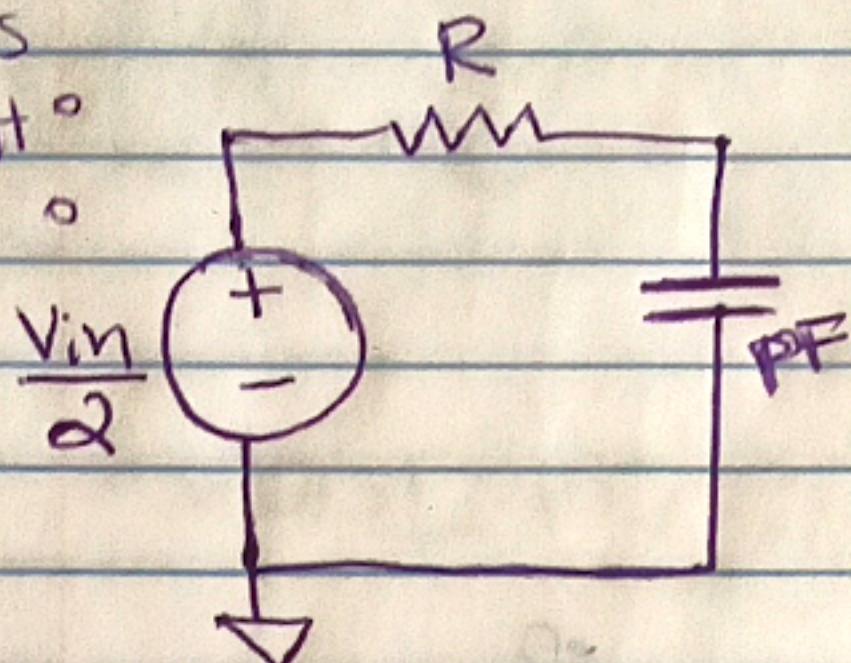

Time Delay^o
 $t_d = R_{TH} (C_{load}) (0.7RC)$

$$= R(10\text{pF})(0.7RC)$$

here $R = 10\text{k}$

$$= (10\text{k}\Omega)(10\text{pF})(0.7RC)$$

$$= 70\text{nsec}$$